

B.Tech II Year II Semester (R13) Regular & Supplementary Examinations May/June 2016

PULSE & DIGITAL CIRCUITS

(Common to ECE and EIE)

Time: 3 hours

Max. Marks: 70

PART – A
(Compulsory Question)

- 1 Answer the following: (10 X 02 = 20 Marks)
- What is meant by linear wave shaping?
 - How can an uncompensated attenuator be modified as a compensated attenuator?
 - List the applications of voltage comparators.
 - State Clamping circuit theorem.
 - What is the main advantage of an emitter-coupled monostable multivibrator over collector-coupled monostable multivibrator?
 - What is meant by loading in a bistable multivibrator?
 - Draw a current sweep circuit.
 - Define the terms phase delay and phase jitter.
 - List the applications of sampling gates.
 - List the disadvantages of ECL.

PART – B


(Answer all five units, 5 X 10 = 50 Marks)

UNIT – I

- 2 (a) A ramp $V_i = \alpha t$ is applied as input to a low-pass RC circuit. Derive the expression for the output voltage. And also draw the typical waveforms.
- (b) A 20 KHz square wave is applied to a RC differentiating circuit, with $R = 4 \text{ K}\Omega$, it produces the output with a tilt of 5%. Calculate the value of the capacitor and lower 3-dB frequency.

OR

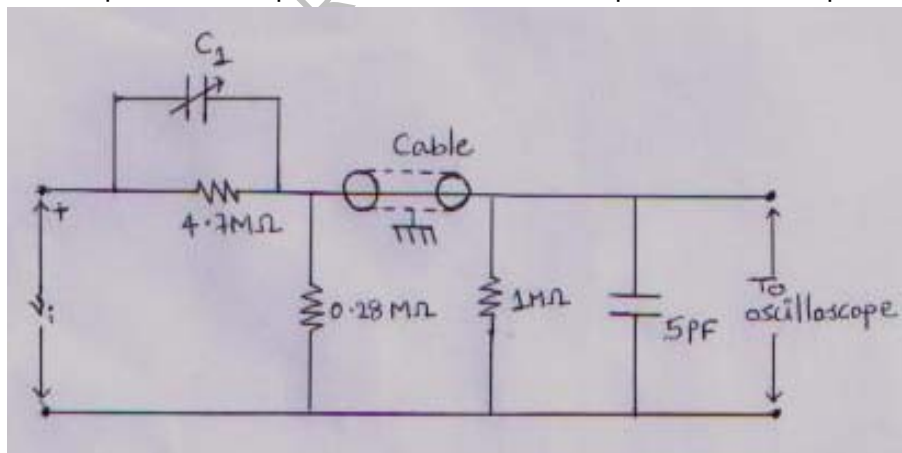
- 3 (a) Derive the expression for percentage tilt, 'P' when a square wave is input to a high-pass RC circuit.
- (b) An oscilloscope test probe shown below has a cable capacitance of 50pF. The input impedance of oscilloscope is $1 \text{ M}\Omega$ in parallel with 5pF. Find the value of the capacitor for better performance.



Contd. in page 2

UNIT – II

 - 4 (a) For the two-level clipper in Figure below, the input varies linearly from 0 to 150 V. Plot the transfer characteristic and obtain the output voltage. Assume ideal diodes.




- (b) What is meant by synchronized clamping?

OR

- 5 (a) Explain the effect of diode characteristics on clamping voltage.
(b) Discuss any two applications of voltage comparators.

UNIT – III

- 6 In a Schmitt trigger circuit shown below, with two 7N4418 n-p-n epitaxial planar silicon transistors, the h_{FE} of the transistors is 70. The circuit is energized from a power supply voltage $V_{CC} = 10\text{ V}$. The resistors in the circuit are $R_s = 3.3\text{ k}\Omega$, $R_{C1} = 2.2\text{ k}\Omega$, $R_{C2} = 820\text{ }\Omega$, $R_1 = 1.8\text{ k}\Omega$, $R_2 = 6.8\text{ k}\Omega$ and $R_e = 4.7\text{ k}\Omega$. Determine the two voltages associated with upper-tripping point and lower-tripping point.

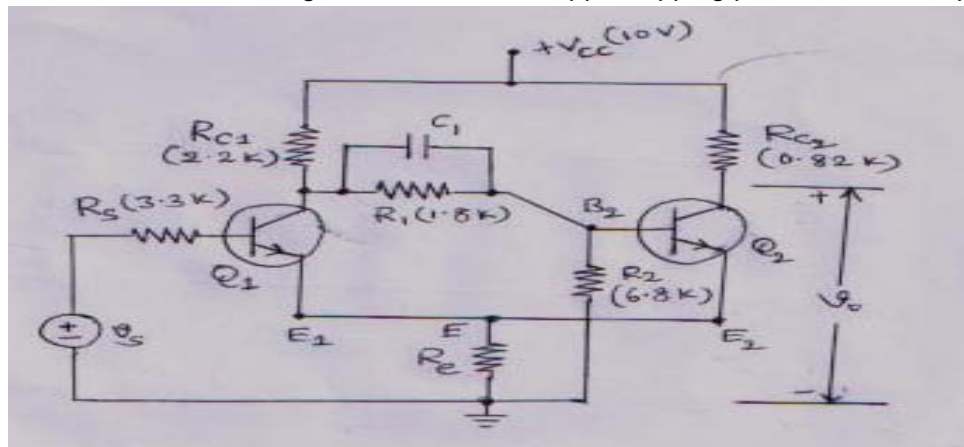

OR

- 7 (a) Draw and explain the operation of collector-coupled astable multivibrator.
(b) Distinguish between symmetrical triggering and unsymmetrical triggering.

UNIT – IV

- 8 (a) Define the three errors that specify deviation from linearity.
(b) Explain the basic principle of a bootstrap sweep generator. Draw the circuit and explain its operation.

OR

- 9 (a) Explain the synchronization of a sweep circuit with symmetrical signals.
(b) Write a brief note on frequency division in a sweep circuit.

UNIT – V

- 10 (a) Draw the circuit of a bidirectional sampling gate and derive the expression for its gain.
(b) Explain about reduction of pedestal in a gate circuit.

OR

- 11 (a) With a neat sketch explain the working of a DTL NAND gate.
(b) Compare various logic families.
