

Code: 9A02305

**R09/SS**

B.Tech II Year I Semester (R09/R13) Supplementary Examinations June 2016

**ELECTRICAL CIRCUITS**

(Common to EEE, EIE, E.Con.E, ECE &amp; ECC)

Time: 3 hours


Max. Marks: 70

Answer any FIVE questions


All questions carry equal marks

\*\*\*\*\*

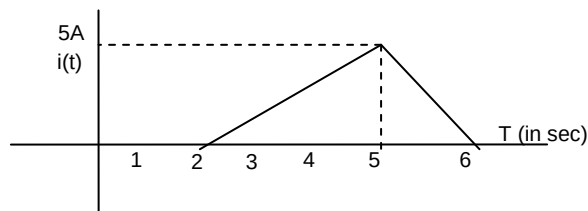- 1 (a) Write a note on inductor and V-I relationship associated with it.  
 (b) A current  $i(t)$  is applied to an inductance ( $L$ ) of 2H as shown in figure below. Find  $V_L(t)$ .



- 2 (a) The expressions for  $n$  resistances connected in parallel.  
 (b) A 20 V battery with an internal resistance of 5 ohms is connected to a resistor of  $x$  ohms. If an additional resistance of 6 ohms is connected across the battery, find the value of  $x$  so that the external power supplied by the battery remains the same.
- 3 (a) What is the concept of effective value of an alternating quantity? What is its practical significance?  
 (b) A series RL circuit has  $R = 25$  ohm and  $X_L = 32$  ohm. It is connected in parallel to a capacitor of 100 micro farads and the combination is connected across a 200 V, 50 Hz supply. Find the current in each branch. Draw the vector diagram showing the total current.
- 4 (a) Give the expression of frequency at which the voltage across the capacitor is maximum.  
 (b) A RC series circuit with  $R = 50$  ohms and  $C = 20$  micro farads is connected parallel to an inductance. The parallel combination is excited by a source of 10 V, 1 kHz. Determine the value of inductance if no reactance current is taken from the supply.
- 5 (a) Derive the expression for equivalent inductance of two coils connecting in series aiding.  
 (b) For the network shown in figure below, find the drop across load resistance  $R_L$ .

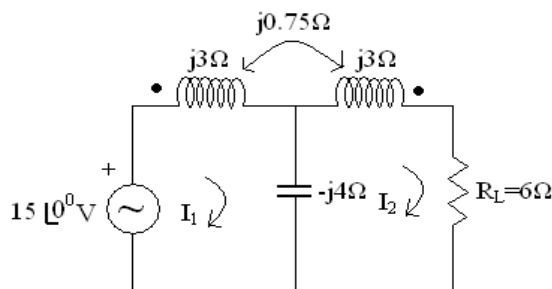


Contd. in page 2


R09/SS

Code: 9A02305

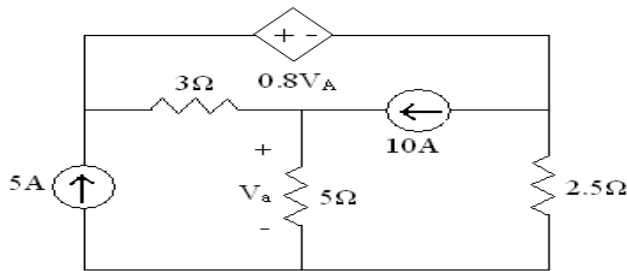
- 6 (a) Explain the concept of duality.  
 (b) With the help of nodal analysis, find power dissipated by all the resistors in the circuit shown below.



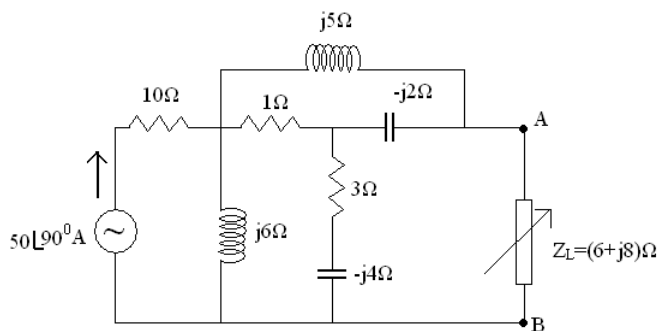- 7 (a) Write limitations of maximum power transfer theorem.  
 (b) Using suitable theorem, calculate voltage across  $Z_L$  for the circuit shown.



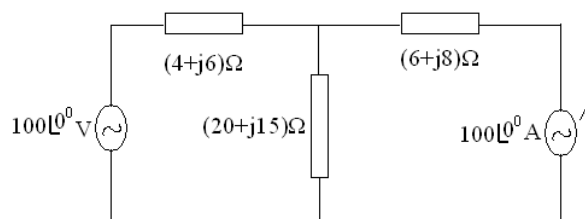- 8 Find the current through  $(4+j6) \Omega$  impedance using superposition theorem and verify it using mesh analysis.



\*\*\*\*\*