

Code: 9A02406

R09

B.Tech II Year II Semester (R09) Supplementary Examinations May/June 2016

NETWORK THEORY

(Electrical & Electronics Engineering)


Time: 3 hours

Max. Marks: 70

Answer any FIVE questions


All questions carry equal marks

- 1 (a) Derive the relation between phase and line values of a three phase delta connected balanced system.
(b) Three inductive coils, each with a resistance of $15\ \Omega$ and an inductance of $0.03\ \text{H}$ are connected in star to three phase, $400\ \text{V}$, $50\ \text{Hz}$ supply. Calculate: (i) Phase current and line current. (ii) Total power absorbed.
- 2 A $3\text{-}\Phi$ $400\ \text{V}$ load has p.f of 0.6 lagging. The two wattmeters read a total input of $20\ \text{kW}$. Find the readings of each wattmeter. Derive the expression for power factor.
- 3 The switch in the circuit shown in figure below, is moved from position (1) to (2) at $t = 0$. Find the expression for V_C and V_R for $t > 0$.

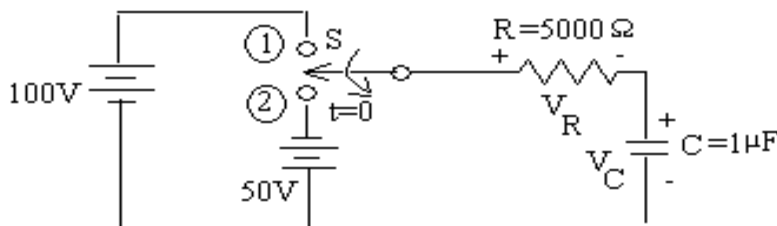

- 4 Derive the expression for $i(t)$ in a series R-C circuit is excited with a sinusoidal voltage source $V = V_m \sin(\omega t + \Phi)$, when the switch is closed at time $t = 0$.
- 5 Construct a circuit that realizes the following parameters:
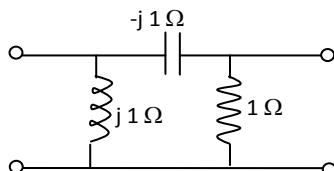
$$[Z] = \begin{bmatrix} 10 & 4 \\ 4 & 6 \end{bmatrix}$$
- 6 Determine the Z-parameters of the two-ports shown below:



- 7 Obtain the exponential Fourier series for $f(t) = t$, $-1 < t < 1$ with $f(t + 2n) = f(t)$.
- 8 Calculate the fraction of the total energy dissipated by a $1\ \Omega$ resistor in the frequency band $-10 < \omega < 10$ rad/sec when the voltage across it is $v(t) = e^{-2t}u(t)$.
