

R09**Code: 9A04306**

B.Tech II Year I Semester (R09) Supplementary Examinations June 2016

DIGITAL LOGIC DESIGN

(Computer Science & Engineering)

Time: 3 hours

Max. Marks: 70

Answer any FIVE questions

All questions carry equal marks

- 1 (a) Apply the number conversions from one system to other using its base:
(i) $(344.25)_{10} = ()_2$.
(ii) $(1001110.01)_2 = ()_{10}$.
(iii) $(CDEF)_{16} = ()_2$.
(iv) $(572)_8 = ()_{16}$.
(b) Given the binary numbers $X = 1110110$ and $Y = 1100010$. Perform the subtraction $X-Y$ and $Y-X$ using complements.
- 2 (a) Realize basic logic gates using Universal gates.
(b) Simplify the following expression $Y = (A+B)(A+C')(B'+C')$.
- 3 Simplify the following Boolean function, using five variable maps:
 $F(A,B,C,D,E) = \Sigma(0,1,4,5,16,17,21,25,29)$
- 4 (a) Design a 4-bit adder-subtractor circuit and explain the operation in detail.
(b) Design a 4x1 multiplexer and explain the working.
- 5 Explain the working of the following:
(a) J-K flip-flop.
(b) S-R flip-flop.
(c) D-flip-flop.
- 6 Explain the design of a 4-bit binary counter with parallel load in detail.
- 7 Design a combinatorial circuit using ROM and PLA. The circuit accepts 3-bit number and generates output binary number equal to square of input number.
- 8 An asynchronous sequential circuit has two internal states and one output. The excitation and output functions describing the functions are:
 $Y_1 = x_1x_2 + x_1y_2' + x_2'y_1$.
 $Y_2 = x_2 + x_1y_1'y_2 + x_1'y_1$.
 $Z = x_2 + y_1$.
Implement the circuit defined above with NAND SR latches.
