

II B.Tech I Semester(RR) Supplementary Examinations, May/June 2010

LINEAR AND DIGITAL IC APPLICATION

(Common to Computer Science & Engineering, Information Technology and Computer Science & Systems Engineering)

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
All Questions carry equal marks

1. (a) List out the ideal characteristics of an OP-AMP. [3]
(b) With neat block diagram explain the function of various building blocks of an OP-AMP. [10]
(c) Draw the equivalent circuit of an OP-AMP. [3]
2. (a) Classify the types of OP-AMP based multipliers. How a multiplier can be used to [8]
 i. double the incoming frequency
 ii. detect the phase angle of a signal
(b) Design a subtractor in non inverting configuration [8]
3. (a) What is a switching regulator? Draw the block diagram of a typical switching regulator and explain its operation. [8]
(b) What are the four types of voltage regulators? Compare the performance of these regulators. [8]
4. (a) Explain the operation of Astable multivibrator using 555 timer. [10]
(b) Design a square waveform generator of frequency 1kHz and duty cycle of 75% using 555 timer. [6]
5. Explain the terms Lock range, Capture range and Pull-in time a PLL. How are Lock ranges and Capture range determined? [16]
6. (a) Explain the term "Frequency Sealing" with suitable example. [6]
(b) Design a wide band-pass filter with $f_L=200Hz$, $F_H=1KHz$ and a pass-band gain=4. Draw the frequency response and calculate 'Q' factor for the filter. [10]
7. (a) Define the following terms : [4]
 i. Fan-in
 ii. Fan-out
 iii. Standard load
 iv. Noise-Margin.
(b) Draw the circuit ECL OR/NOR gate and explain its operations with the help of Truth Table. [8]
(c) What are the principal advantages of ECL logic (List out at least 5 advantages) [4]
8. (a) What are the basic blocks of analog multiplexer? Explain how the data selection process is performed in it. [8]
(b) Draw a sample and hold circuit and explain its operation with necessary input and output waveforms and indicate its uses. [8]
