

Code :9A02306

R9

II B.Tech I Semester(R09) Supplementary Examinations, May 2011
BASIC ELECTRICAL ENGINEERING


(Computer Science and Engineering, Information Technology, Computer Science & Systems
 Engineering)

Time: 3 hours

Max Marks: 70

Answer any FIVE questions
 All questions carry equal marks

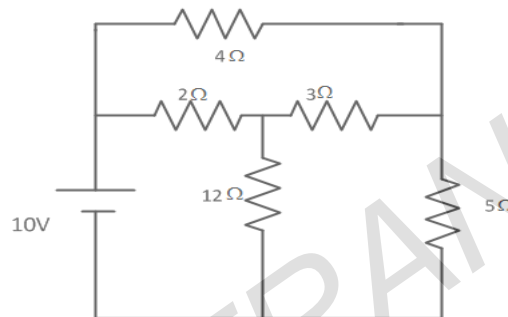- State and explain ohm's law
 - Three resistances 2Ω , 4Ω and 6Ω are connected in series across a voltage supply voltage across 2Ω resistor is $4V$. Find the voltage across remaining resistances and total voltage.
- State and explain superposition theorem
 - Find the current supplied by $10V$ battery by using star-Delta transformation.



- Derive an expression for average value of an AC current wave form $I = E_m \sin \theta$
 - An alternating current is expressed as $I = 14.14 \sin 314t$. Determine.
 - Maximum current
 - rms current
 - Frequency
 - Instantaneous current when $t = 0.02\text{msec}$.
- Define efficiency and Regulation. Explain how will you pre-determine the efficiency and regulation with neat circuit diagrams.
- Explain the principle of operation of DC generator
 - A lap wound DC generator having 80 slots with 10 conductors per slot generator at no load emf of $400V$, when running at 1000 rpm . At what speed should it be rotated to generate a voltage of $220V$ on open circuit.
- Derive the torque equation of a DC motor
 - A $100V$ series motor taken $45A$ when running at 750 rpm . Its armature resistance is 0.22 ohm while the series field resistance is 0.13 ohms Iron and frictional losses amounts to $750W$. Find the shaft power.
- Explain with the help of diagram how a rotating magnetic field is produced in a 3- phase Induction Motor.
 - A 3-phase, 6 pole, 50HZ induction motor develops 4 KW including friction and windage losses at 950 rpm . If the stator loss is $250W$. find the rotor frequency.
- Explain the construction and operation of permanent magnet moving coil instruments with a neat diagram.
