

Code :RR311003

RR

III B.Tech I Semester(RR) Supplementary Examinations, May 2011
LINEAR & DIGITAL IC APPLICATIONS

(Electronics & Instrumentation Engineering, Biomedical Engineering, Electronics & Control Engineering)

Time: 3 hours

Max Marks: 80

Answer any FIVE questions
All questions carry equal marks

1. (a) Define the terms : SVRR, CMRR, input bias current, input offset voltage, Gain Bandwidth product.
- (b) What are the differences between the inverting and non inverting terminals? What do you mean by the term 'virtual ground'?
2. (a) Design a unity gain summing amplifier to add three dc input voltages -0.5V, 0.1V and 0.75V in inverting configuration. If the saturation voltages of the OP-AMP are +18V, and -18V, find the possible maximum gain of the amplifier.
- (b) Design a subtractor circuit whose output is equal to the difference between the two inputs. Use a differential OP-AMP configuration.
3. (a) What feedback is preferred for oscillators and why? What is the effect of negative feedback?
- (b) Design an OP-AMP based relaxation oscillator and derive the frequency of oscillation.
4. (a) Draw the circuit of Schmitt trigger using 555 timer and explain its operation.
- (b) How is an Astable multivibrator using 555 timer connected in to a pulse position modulator?
5. Explain the operation of the following blocks of PLL in detail
 - (a) Analog and Digital phase detectors
 - (b) Voltage controlled oscillator
 - (c) Low Pass-Filter.
6. (a) Explain the operation of a delay equalizer circuit with neat sketches. Derive an expression relating input and output voltages of the equalizer.
- (b) For the all pass filter, determine the phase shift between input and output at $f=2$ kHz. To obtain a positive phase shift. What modifications are necessary in the circuit?
7. (a) Compare different logic families and mention their advantages and disadvantages.
- (b) Which is the fastest non-saturated logic gate ? Draw the circuit and explain its functions.
8. (a) List out and compare different types of A/D converters.
- (b) Give the schematic circuit diagram of the fastest A/D converter and explain its operation.
