

Code :EE3221

RA

III B.Tech II Semester(R05) Supplementary Examinations, April/May 2011
ANALYSIS OF LINEAR SYSTEMS
(Electrical & Electronics Engineering)

(For students of RR regulation readmitted to III B.Tech II Semester R05)

Time: 3 hours

Max Marks: 80

Answer any FIVE questions
All questions carry equal marks
 ★ ★ ★ ★ ★

1. (a) Distinguish between translational and rotational mechanical system with suitable examples and develop the analogous relationships between various quantities of these systems.
- (b) Develop the force-current analogous circuit for the system shown in figure 1 and hence develop the nodal equations.

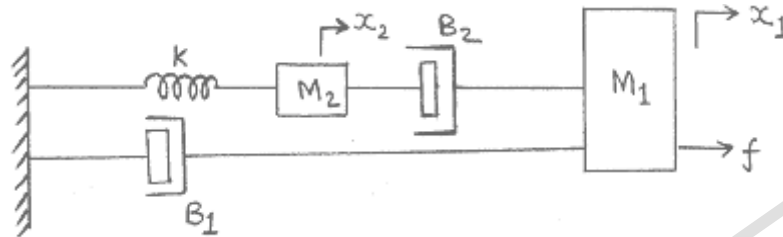


Figure 1:

2. (a) The transfer function of a system is $G(s) = \frac{2}{(s+1)(s+2)}$ obtain the state variable representation of the systems.
- (b) Determine the state transition matrix for the system represented by the characteristic matrix $A = \begin{bmatrix} 3 & 0 & 0 \\ 0 & -2 & 1 \\ 1 & 4 & 1 \end{bmatrix}$
3. (a) Find the current $i(t)$ in a series R-L-C circuit comprising of resistor $R = 5\Omega$, $L=1H$, $C= \frac{1}{4} F$ when the step voltage $3 u(t-3)$ is applied to it
- (b) Find the response of a series R-C circuit with $R=1\Omega$, $C=2F$ with an impulse voltage of $2\delta(t-3)$ applied across it.
4. (a) State and Explain the graphical interpretation of convolution theorem.
- (b) Determine the convolution integral for the functions $(e^{-2t}) (\sin 2t)$
- (c) Given that impulse response of a systems is $\frac{s}{s+1}$, find the response for an input of e^{-2t} .
5. A full-wave rectified output voltage, with an input voltage of 230 V, 50Hz, is applied to a series R-L circuit with $R=2\Omega$, $L = 3.18mH$. Find:
 - (a) Fourier coefficients
 - (b) RMS value of voltage
 - (c) RMS value of current
 - (d) Average power consumed in the circuit and power factor of the load.
6. (a) Find the signal $f(t)$ whose Fourier transform is $F(j\omega) = 5/(6 + j5\omega - \omega^2)$
- (b) Find the Fourier transform of the following functions:
 - i. $f(t) = te^{-at}$ for $t \geq 0$
 - ii. $V(t) = V_m \cos t - \Pi/2 \leq t \leq \Pi/2$
 $= 0$ elsewhere
7. (a) Check whether the following polynomial is Hurwitz or not?
 $H(s) = s^4 + 2s^2 + 3s + 6$
- (b) Find the range of values of 'a' so that $H(s) = s^4 + s^3 + as^2 + s + 3$ is Hurwitz.
8. (a) For the following driving point input impedance, synthesize the realizable impedance with R-L elements using Fosters first form:
 $Z(s) = (s+2)(s+4)/(s+3)(s+5)$
- (b) Synthesis the given function
 $Z(s) = 2(s+1)(s+5)/s(s+3)$
 into two R-C parallel branches and hence determine the values of branches $R_1 - C_1$ and $R_2 - C_2$ and assume $R_1 = R_2$.

★ ★ ★ ★ ★