

Code :RR320201

RR

III B.Tech II Semester(RR) Supplementary Examinations, April/May 2011
ANALYSIS OF LINEAR SYSTEMS
 (Electrical & Electronics Engineering)

Time: 3 hours

Max Marks: 80

Answer any FIVE questions
 All questions carry equal marks

- Distinguish between continuous and discrete time systems with suitable examples.
 - Explain the D'Alembert's Principle with the help of a suitable mechanical translational systems.
 - For the mechanical system shown in figure1, draw the mechanical equivalent network. Hence develop the force-voltage analogous electric circuit and write the equations.

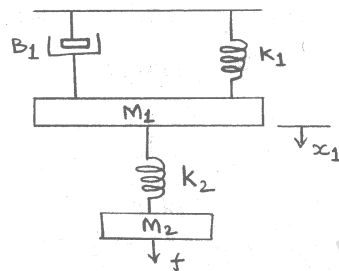


Figure 1:

- The transfer function of a system is $G(s) = \frac{2}{(s+1)(s+2)}$ obtain the state variable representation of the systems.
 - Determine the state transition matrix for the system represented by the characteristic matrix $A = \begin{bmatrix} 3 & 0 & 0 \\ 0 & -2 & 1 \\ 1 & 4 & 1 \end{bmatrix}$
- Find the current $i(t)$ in a series R-L-C circuit comprising of resistor $R = 5\Omega$, $L=1H$, $C= \frac{1}{4} F$ when the step voltage $3 u(t-3)$ is applied to it
 - Find the response of a series R-C circuit with $R=1\Omega$, $C=2F$ with an impulse voltage of $2\delta(t-3)$ applied across it.
- Find the response $i(t)$ for a series R-C circuit, with $R = 1\Omega$, $C=1F$ and applied by a periodic waveforms shown in figure 2 Assume initial conditions to be zero.
 - Find the inverse Laplace transform of the following function using convolution theorem $F(s) = \frac{4s}{(s+2)(s^2+1)}$

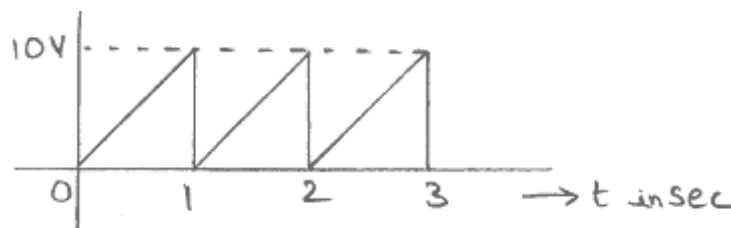


Figure 2:

- A full-wave rectified output voltage, with an input voltage of 230 V, 50Hz, is applied to a series R-L circuit with $R=2\Omega$, $L = 3.18mH$. Find:
 - Fourier coefficients

- (b) RMS value of voltage
 (c) RMS value of current
 (d) Average power consumed in the circuit and power factor of the load.
6. (a) Find the Fourier transform of a gate function

$$G(t) = \begin{cases} 1 & \text{for } -\frac{T}{2} < t < \frac{T}{2} \\ 0 & \text{otherwise} \end{cases}$$
- (b) Find the Fourier transform of the constant signal $f(t) = A(-\infty < t < \infty)$
7. (a) Test whether the following polynomial is Hurwitz or not?
 $H(s) = s^6 + 5s^5 + 13s^4 + 21s^3 + 20s^2 + 16s + 8$
- (b) Test whether the following function is positive real or not?
 $F(s) = (s^2 - 2s + 2)(s^2 - 6s + 9)/(s^2 + 2s + 2)(s^2 + 6s + 9)$
8. (a) Explain how the removal of pole at infinity of an impedance $Z(s)$ can realize an element in the network.
- (b) Realize the network with the following driving point impedance function using first Foster form.
 $Z(s) = (s+2) / s(2s+5)$
