

Code: R5102303

R05

B. Tech I Year (R05) Supplementary Examinations, May 2012
BASIC ELECTRICAL & ELECTRONICS ENGINEERING
(Biotechnology)

Time: 3 hours

Max Marks: 80

Answer any FIVE questions
All questions carry equal marks

- 1 (a) State and explain Kirchoff's laws.
(b) A reactor having negligible resistance and an inductance of 0.1 H is connected in series with a resistor of 15Ω . The circuit is connected across 230 V, 50 Hz, single phase AC supply find:
(i) Current flowing in the circuit.
(ii) Power factor of the circuit.
(iii) Voltage across the reactor and resistor.
- 2 (a) Explain the principle of operation of single phase transformer.
(b) Explain the principle of operation of single phase induction motors.
- 3 (a) Explain the principle and operation of moving coil instruments with neat diagram.
(b) Explain the operating principle of dynamometer type wattmeters with neat diagram.
- 4 Explain the operation of zener diode. Also explain its characteristics.
- 5 Explain the operation of bipolar junction transistor. Also explain its characteristics.
- 6 Explain class A power amplifier in detail.
- 7 Write short notes on:
(a) Adder.
(b) Multiplier.
(c) Integrator.
(d) Differentiator.
- 8 Explain in detail the various types of Flip Flops.
