

R7

Code: R7 210102

B.Tech II Year I Semester (R07) Supplementary Examinations, May 2012

ELECTRICAL AND ELECTRONICS ENGINEERING

(Common to CE and ME)

Time: 3 hours

Max Marks: 80

Answer any FIVE questions

All questions carry equal marks

- 1 (a) Define and explain Kirchhoff's laws
(b) Two resistances of $1.5\ \Omega$ and $3.5\ \Omega$ are connected in parallel and their combination is connected in series with a resistance of $1.95\ \Omega$. Find the equivalent resistance of the circuit. What current will it draw if connected to a 30V supply?
- 2 (a) Explain the principle of operation of DC generator.
(b) A 220V, DC shunt motor takes a total current of 100 A and runs at 750 rpm. The resistance of the armature winding and shunt field winding are $0.1\ \Omega$ and $40\ \Omega$ respectively. Find the torque developed by armature.
- 3 (a) Derive the emf equation of single phase transformer.
(b) A single phase transformer working at unity power factor has an efficiency of 90% at half load and full load of 500 W. Determine the efficiency at 75% of full load.
- 4 (a) Explain the principle of operation of 3 phase induction motor.
(b) Explain the slip- torque characteristics of 3-phase induction motors.
- 5 Explain the principle and operation of permanent magnet moving coil instrument with neat diagram.
- 6 (a) Explain V-I characteristics of P-N junction diode.
(b) Explain the operation of half wave and full wave rectifiers with neat circuit diagrams.
- 7 Explain the characteristics of SCR in detail.
- 8 (a) Derive the expression for the electrostatic deflection of CRO.
(b) Explain how voltage and frequency can be measured by using CRO.
