

Code: R7310202

III B. Tech I Semester (R07) Supplementary Examinations, May 2012

**ELECTRICAL MEASUREMENTS**  
(Electrical & Electronics Engineering)

Time: 3 hours

Max Marks: 80

Answer any FIVE questions  
All questions carry equal marks

\*\*\*\*\*

- 1 (a) How the electrical measuring instruments are classified?  
(b) A moving coil instrument has a resistance of  $10\ \Omega$  and gives a full-scale deflection when carrying 50mA. Show how it can be adopted to measure voltage up to 750 V and current 100 A.
- 2 (a) Explain the advantages of instrument transformers.  
(b) A current transformer has a single turn primary and a 200 turns secondary winding. The secondary winding supplies a current of 5 A to a non-inductive burden of  $1\ \Omega$  resistance. The requisite flux is set up in the core by an mmf of 80 A. The frequency is 50 Hz and the net cross-section of the core is  $1000\ \text{mm}^2$ . Calculate the ratio and phase angle of the transformer. Also, find the flux density in the core. Neglect the effects of magnetic leakage, iron losses and  $I^2R$  losses.
- 3 A dynamometer wattmeter is used to measure the power factor of a  $20\ \mu\text{F}$  capacitor. The pressure coil of the wattmeter having a resistance  $1000\ \Omega$  and inductive reactance of  $15\ \Omega$  is connected across a 50 Hz supply. The current coil of the wattmeter, a variable resistor R and a capacitor are connected in series across the same supply. The wattmeter deflection is made zero by adjusting the value of R to  $1.65\ \Omega$ . If the current coil resistance is  $0.1\ \Omega$  and its inductance is negligible; determine the power factor of the capacitor
- 4 Enumerate the different type of tests that are to be carried out on a 1-  $\Phi$  induction type watt-hour meter. Describe the long period dial test.
- 5 (a) What are the differences between D.C and A.C potentiometers?  
(b) What are the practical difficulties associated with A. C potentiometers?  
(c) How the D.C potentiometers are standardized?
- 6 (a) Describe the substitution method of measurement of medium resistances and list the factors on which the accuracy of the method depends.  
(b) A Kelvin bridge is balanced with the following constants. Outer ratio arm  $100\ \Omega$  and  $1000\ \Omega$ ; inner arms ratio  $99.92\ \Omega$  and  $1000.6\ \Omega$ ; resistance of link  $0.1\ \Omega$ ; standard resistance  $0.00377\ \Omega$ . Calculate the value of unknown resistance.
- 7 (a) Draw and explain high voltage Schering bridge with a neat circuit diagram.  
(b) What are the special features of high voltage Schering bridge?
- 8 Explain the construction and working of a ballistic galvanometer.

\*\*\*\*\*