

Code: 9A02504

III B. Tech I Semester (R09) Supplementary Examinations, May 2012

POWER ELECTRONICS

(Common to Electrical & Electronics Engineering & Electronics & Control Engineering)

Time: 3 hours

Max Marks: 70

Answer any FIVE questions
All questions carry equal marks

- 1 (a) Explain the operation of SCR using schematic diagram and explain the importance of junctions.
(b) Discuss the conditions which must be satisfied for turning on an SCR with a gate signal.
- 2 Explain the R-C triggering circuit with suitable waveforms.
- 3 (a) Explain, the half-waving effect in a single-phase symmetrical half controlled converters.
(b) A voltage source $e=100 \sin 377 t$ supplies a resistive load of 100 ohm through a thyristor, which performs half-wave controlled rectification. Calculate the average power in the load, if the firing angle is fired at 45 deg. With respect to the supply voltage waveform.
- 4 (a) Explain the effect of freewheeling diode in detail. Also justify the statement "Freewheeling diode improves the power factor of the system".
(b) A single phase fully controlled bridge is connected to an a.c supply of 230 V and 50 Hz is used for the speed control of dc motor with separate field excitation. The full load average armature current is 10 A and the converter operates at a firing angle $\alpha=\pi/4$. Neglecting the inductance and resistance of both armature and source, calculate the minimum value of series inductance, L_d required in the armature circuit to provide for continuous current conduction.
- 5 (a) Describe the working principle of continuous mode of three phase 3-pulse converters with associate waveforms at firing angle 60° .
(b) What are the advantages of freewheeling diode?
- 6 (a) List the advantages and disadvantages of Triac over SCR.
(b) List the main features of Triac.
- 7 (a) Describe the Morgan chopper with associated voltage and current waveforms.
(b) Enumerate the merits of Morgan chopper compared to Jones chopper.
- 8 (a) Explain the operation of 1-phase modified Mc Murray half bridge inverter with neat diagram.
(b) The 1-phase modified Mc Murray half bridge inverter is fed by a dc source of 230 V. The dc source voltage may fluctuate by $\pm 10\%$. The current during commutation may vary from 30 to 120 A. Determine the values of the commutating components if the thyristor turn off time is 10 μs . Also compute the values of R.
