

Code: R7221303

R07

B.Tech II Year II Semester (R07) Supplementary Examinations, April/May 2013

ELECTRICAL & ELECTRONICS MEASUREMENTS

(Electronics & Control Engineering)

Time: 3 hours

Max. Marks: 80

Answer any FIVE questions
All questions carry equal marks

- 1 (a) Explain the types of construction used to extend the scale span of PMMC instrument to say about 240° to 300° . Draw neat diagrams to illustrate your answers.
(b) Describe how a potential divider arrangement is used for multiplies in the case of multi-range voltmeters. Derive expressions for resistance for different sections for 4-range voltmeter.
- 2 (a) Describe the circuit diagram of a series type ohmmeter. Explain how it is designed. What is the significance of half scale value?
(b) Describe the constructional details and working of an electro-dynamometer instrument. Derive the equation for deflection under a.c operation if the meter is spring controlled.
- 3 (a) Explain how power can be measured in a 3 phase circuit with the help of two watt meters. Illustrate your answer with the help of a phasor diagram for a balanced star connected load.
(b) Define the following terms as used for instrument transformers:

(i) Transformation ratio	(iv) Ratio correction factor
(ii) Nominal ratio	(v) Burden
(iii) Turns ratio	

Use specific examples to illustrate your answer.
- 4 (a) Describe the circuit diagram and operation of a triac rms reading voltmeter using thermocouples. Explain how these waveforms are free from waveform errors.
(b) Explain the circuit diagram of following types of electronic voltmeter:

(i) Voltmeters using series connected diode
(ii) Voltmeters using full wave bridge rectifier
- 5 (a) Derive the expression for vertical deflection of electron beam in CRT.
(b) Describe the principle of working and circuit diagram of a digital oscilloscope.
- 6 (a) Describe the circuit and working of a Q meter. Derive the equations.
(b) Describe the methods of measurement voltage of radio frequencies.
- 7 (a) Describe the circuit diagram and working of a laboratory type square wave generator.
(b) With a neat block diagram explain the operation of a spectrum analyzer.
- 8 (a) Describe with the help of a circuit diagram the working of a universal time counter.
(b) Describe with the help of a suitable circuit diagram, time interval measurements.
