

Code: 9A02406

1

B.Tech II Year II Semester (R09) Regular & Supplementary Examinations, April/May 2013

NETWORK THEORY


(Electrical and Electronics Engineering)

Time: 3 hours

Max Marks: 70

Answer any FIVE questions
All questions carry equal marks

- 1 (a) Write down the advantages of a poly phase system? What is phase sequence? Explain the significance of phase sequence.
- (b) A delta connected 3-phase load has a resistance of $10\ \Omega$ and inductive reactance of $15\ \Omega$ in each phase. It is fed by 3-phase, 440 V, 50 Hz supply. Find
(i) Apparent power. (ii) Active power. (iii) Reactive power.
- 2 Show that in the two-wattmeter method of 3- Φ power measurement, the sum of the readings of the two wattmeters gives the total power consumed in 3- Φ circuit. Hence prove: $\Phi = \tan^{-1}(\sqrt{3}(w_1 - w_2) / (w_1 + w_2))$.
Where Φ is the phase angle of the load and w_1 & w_2 are the readings of the wattmeters.
- 3 (a) Derive the expression for current when a dc voltage V is applied suddenly (i.e. at time = 0) by closing a switch in a series R-L circuit.
- (b) In the circuit shown in fig below, the switch is in position (1) to establish steady state condition and at $t = 0$, it is switched to position (2). Find the resulting current.

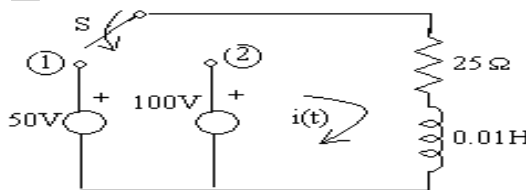


- 4 A series RC circuit with $R = 100\ \Omega$ and $C = 25\ \mu\text{F}$ has a sinusoidal voltage $V = 250 \sin(500t)$. Find the total current assuming that the capacitor is initially uncharged.

Contd. in Page 2


1

Code: 9A02406

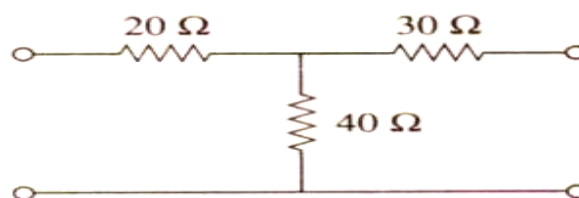- 5 Determine z and y parameters of the network shown below:



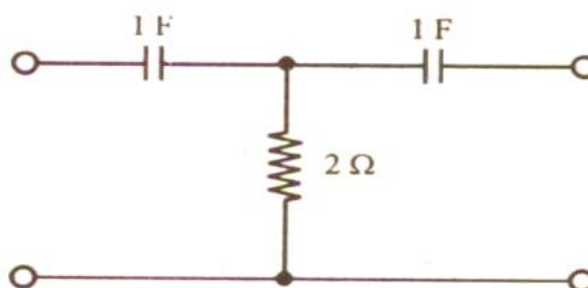- 6 Find the transmission parameters for the network shown below:



- 7 Sketch the diagram of a rectangular pulse train. Derive its Fourier series.
- 8 Discuss the time shifting and frequency shifting properties of Fourier transform.

Code: 9A02406

2

B.Tech II Year II Semester (R09) Regular & Supplementary Examinations, April/May 2013

NETWORK THEORY


(Electrical and Electronics Engineering)

Time: 3 hours

Max Marks: 70

Answer any FIVE questions
All questions carry equal marks

- 1 (a) Derive the relation between phase voltage and line voltage, phase current and line current of a three phase delta connected balanced system.
- (b) Three choke coils each having a resistance of $10\ \Omega$ and inductance $0.019\ \text{H}$ are connected in star across a 3-phase, $415\ \text{V}$, $50\ \text{Hz}$ ac supply. Find (i) Line current (ii) Power factor and (iii) Power input.
- 2 Two wattmeters are used to measure the power input in a $3\text{-}\Phi$ circuit indicate $1000\ \text{W}$ and $500\ \text{W}$ respectively. Find the power factor of the circuit:
 - (i) When both wattmeter readings are positive.
 - (ii) When the latter is obtained by reversing the current coil connections. Derive the expression for power factor.
- 3 (a) Derive the expression for current when a dc voltage V is applied suddenly (i.e. at time $= 0$) by closing a switch in a series R-L circuit.
- (b) In the circuit shown in the below fig. the switch is closed at $t = 0$. Find the values of i_1 , i_2 , di_1/dt , di_2/dt , d^2i_1/dt^2 and d^2i_2/dt^2 at $t = 0^+$.

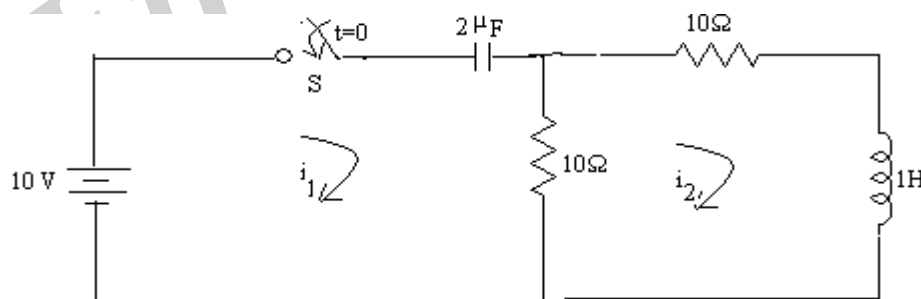


Contd. in Page 2


Code: 9A02406

2

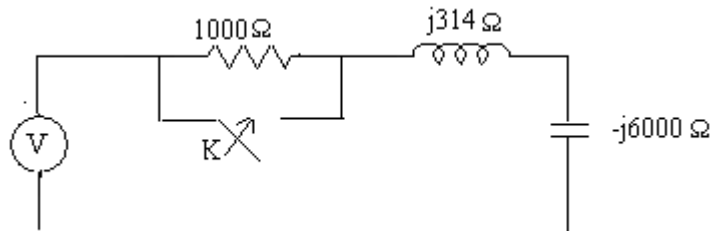
- 4 In fig shown below with switch open, steady state is reached with $V = 100 \sin(314 t)$ volts. The switch is closed at $t = 0$. The circuit is allowed to come to steady state again. Determine the steady state current and complete solution of transient current.



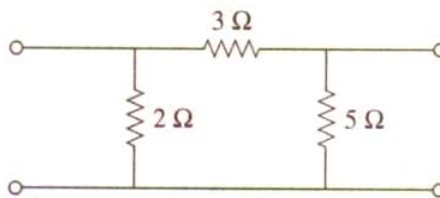- 5 Determine the h-parameters for the circuit shown below:



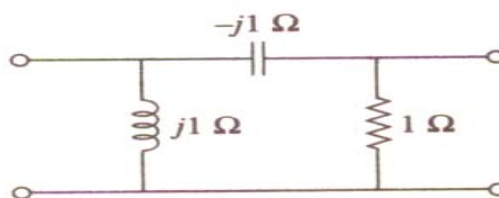- 6 Determine the Z-parameters of the two-ports shown below:



- 7 Sketch the diagram of a saw-tooth wave form. Derive its Fourier series.
- 8 (a) Derive the Fourier transform of the double-sided exponential $e^{-a(t)}$.
- (b) Derive the Fourier transform of saw-tooth pulse, $p(t) = 10 + [u(t) - u(t - 2)]$

Code: 9A02406

3

B.Tech II Year II Semester (R09) Regular & Supplementary Examinations, April/May 2013

NETWORK THEORY


(Electrical and Electronics Engineering)

Time: 3 hours


Max Marks: 70

Answer any FIVE questions
All questions carry equal marks

- 1 (a) Explain the three watt meter method measurement of power with a neat diagram.
(b) Three coils each having a resistance of $20\ \Omega$ and an inductive reactance of $15\ \Omega$ are connected in delta and fed by a 3-phase, 400 V, 50 Hz system.
Find (i) Line current (ii) Power and (iii) Power factor
- 2 A symmetrical 3-phase, 100 V, three wire supply feeds an unbalanced star connected load, with impedances of the load as, $Z_R = 5\angle 0^\circ$, $Z_Y = 2\angle 90^\circ$ and $Z_B = 4\angle -90^\circ$ ohms.
Find the (i) Line currents. (ii) Voltage across the impedances. (iii) The displacement neutral voltage by using star-delta conversion method.
- 3 (a) Obtain the expression for $i(t)$ in a series R-C circuit is excited with a dc voltage source V , when the switch is closed at time $t = 0$.
(b) In the circuit shown in fig below, switch 'K' is closed at $t = 0$. Find the values of i , di/dt and d^2i/dt^2 at $t = 0^+$.

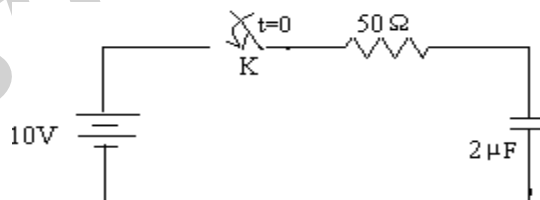

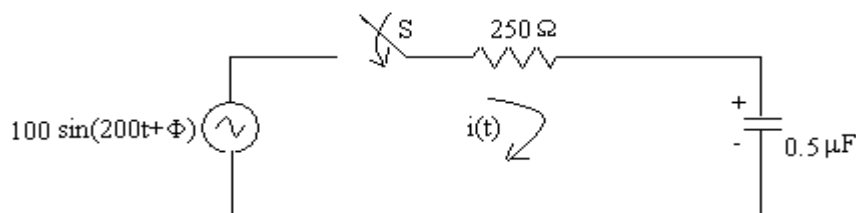- 4 In the RC circuit shown in the fig below, the capacitor has an initial charge $Q_0 = 25 \times 10^{-6}$ C with polarity as shown. A sinusoidal voltage $V = 100 \sin(200t + \Phi)$ is applied to the circuit at a time corresponding to $\Phi = 30^\circ$. Determine the expression for the current $i(t)$.




Contd. in Page 2


3

Code: 9A02406

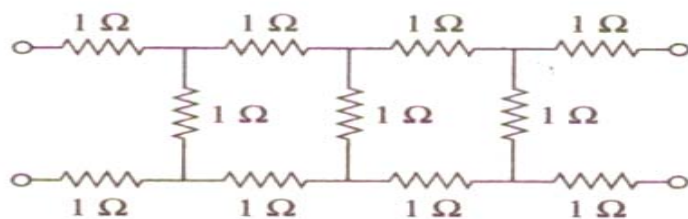- 5 Find the impedance parameters of the network shown below:



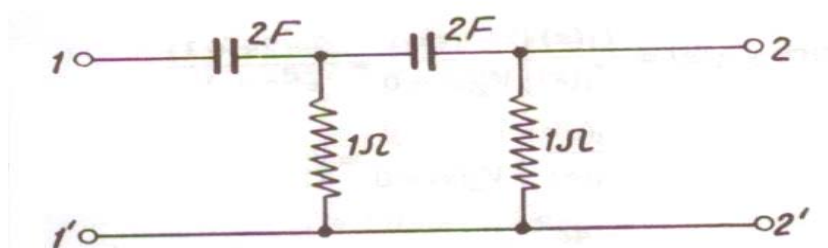- 6 Find the y-parameters for the following network.



- 7 Determine the Fourier series for the half-wave rectified cosine function.
- 8 Discuss the time integration and Frequency differentiation properties of Fourier transform.

Code: 9A02406

4

B.Tech II Year II Semester (R09) Regular & Supplementary Examinations, April/May 2013

NETWORK THEORY


(Electrical and Electronics Engineering)

Time: 3 hours


Max Marks: 70

Answer any FIVE questions
All questions carry equal marks

- 1 (a) Derive the relation between phase and line values of a three phase delta connected balanced system.
- (b) Three inductive coils, each with a resistance of 15Ω and an inductance of 0.03 H are connected in star to three phase, 400 V , 50 Hz supply. Calculate (i) phase current and line current. (ii) total power absorbed.
- 2 Three impedances of $(7 + j4) \Omega$; $(3 + j2) \Omega$ and $(9 + j2) \Omega$ are connected between neutral and the red, yellow and blue phases, respectively of a 3-phase, four wire system. The line voltage is 440 V . Calculate (i) The current in each line and (ii) The current in the neutral wire.
- 3 (a) Derive the expression for $i(t)$ in a series R-C circuit is excited with a dc voltage source V , when the switch is closed at time $t = 0$.
- (b) In the circuit shown in fig below, switch 'K' is closed at $t = 0$. Find the values of i , di/dt and d^2i/dt^2 at $t = 0^+$.

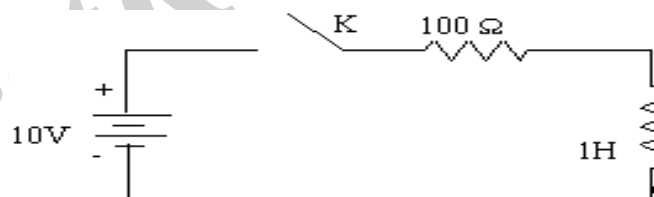

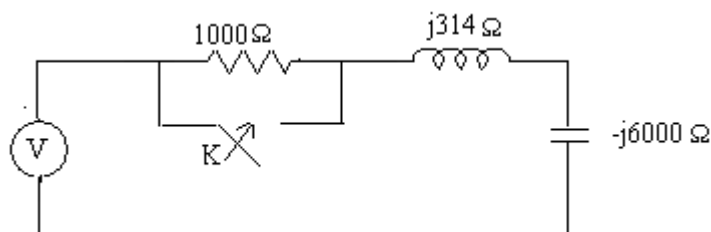- 4 In fig shown below with switch open, steady state is reached with $V = 100 \sin(314t)$ volts. The switch is closed at $t = 0$. The circuit is allowed to come to steady state again. Determine the steady state current and complete solution of transient current by using Laplace transform method.




Contd. in Page 2


4

Code: 9A02406

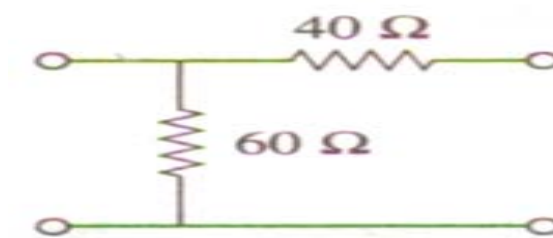- 5 Find the h parameters for the network shown below:



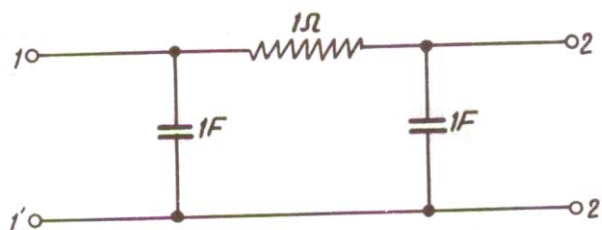- 6 Find ABCD parameters for the following network:



- 7 Derive the Fourier series of a half-wave rectified sine wave.
- 8 Determine the inverse Fourier transform of:
- (a) $F(\omega) = 4\delta(\omega + 3) + \delta(\omega) + 4\delta(\omega - 3)$
- (b) $H(\omega) = 6 \cos 2\omega$
