

R09

Code: 9A04605

B.Tech IV Year II Semester (R09) Advanced Supplementary Examinations, July 2013

VLSI DESIGN

(Electronics and Computer Engineering)

Time: 3 hours

Max. Marks: 70

Answer any FIVE questions
All questions carry equal marks

- 1 Explain clearly about p-well CMOS fabrication process with neat diagrams.
- 2 Mention different non ideal I-V effects and clearly explain about them.
- 3 What are the advantages of scaling? Distinguish between constant field scaling and lateral scaling.
- 4 What is the problem of driving large capacitance load? Explain a method to drive such load.
- 5 (a) Make a comparison between dynamic and static memory cells.
(b) With the help of a diagram explain the architecture and working of memory arrays?
- 6 Explain how does the delay and area grows with the number of data input in a multiplexer.
- 7 (a) By considering a sea of gate array (SOG), design the wiring that would construct a logic function.

$$f = \overline{ABC} + A\overline{B}\overline{C}.$$
(b) Using VHDL as a tool synthesizes the structural design of a RAM.
- 8 (a) What is a level sensitive logic system?
(b) With suitable diagram explain the principle of testing through LSSD approach.
