

**R07**

Code: R7100206

B.Tech I Year (R07) Supplementary Examinations December/January 2015/2016

**ELECTRICAL CIRCUIT ANALYSIS**

(Electrical Electronics Engineering)

(For 2008 regular admitted batch only)

Time: 3 hours


Max. Marks: 80

Answer any FIVE questions

All questions carry equal marks

\*\*\*\*\*

- 1 (a) State and explain Kirchoff's laws.  
(b) Resistors  $R_1 = 10 \Omega$ ,  $R_2 = 20 \Omega$ ,  $R_3 = 30 \Omega$  are connected in star configuration. Find out the equivalent delta configuration.
- 2 (a) State and explain the Faraday's laws of electromagnetic induction.  
(b) Two coupled coils, with  $L_1 = 20 \text{ mH}$ ,  $L_2 = 10 \text{ mH}$  and  $k = 0.50$  are connected four different ways: series aiding, series opposing and parallel with both arrangements of winding sense. Obtain the equivalent inductance of the four connections.
- 3 (a) The current in an RL circuit with  $R = 12 \Omega$  and  $i(t) = 12\sin(900t) + 7\sin(2700t) + \sin(4500t)$ . Determine the effective applied voltage and average power.  
(b) Define resonance and derive the resonant frequency and quality factor for RLC circuit.
- 4 (a) Explain the concept of complex power. Define power factor. What is its significance in electrical circuits?  
(b) A balanced 3-phase star connected load  $8+j6$  ohms per phase is connected to a three phase 230 V supply. Find the line current, power factor, active power, reactive power and total volt-amperes.
- 5 (a) Select a suitable tree and find cut set and tie set matrices for the graph shown in figure below:

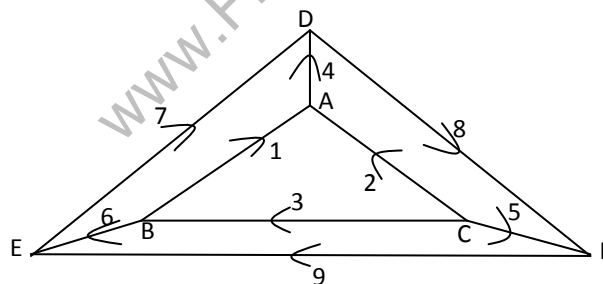


- (b) Explain the principle of duality with an example.

Contd. in page 2

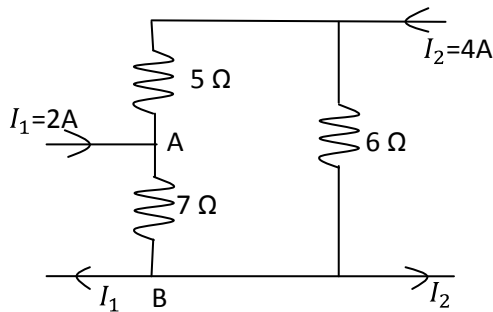
**R07**

Code: R7100206


- 6 (a) State and explain super position theorem.  
(b) Apply super position theorem to the network shown below and find voltage  $V_{AB}$ .



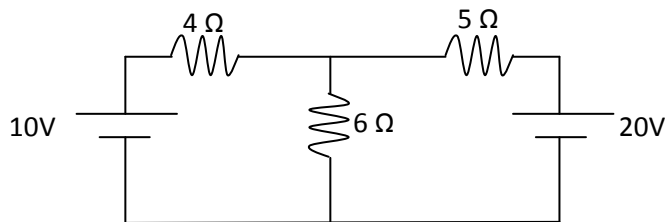- (c) Verify reciprocity theorem for the network shown below.




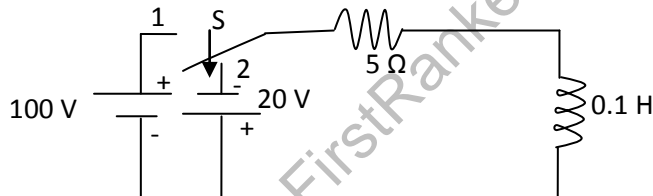- 7 (a) In the circuit shown below, the switch  $S$  is in position 1 for 0.01 seconds and then changed to position 2. Find the time at which the current is zero.



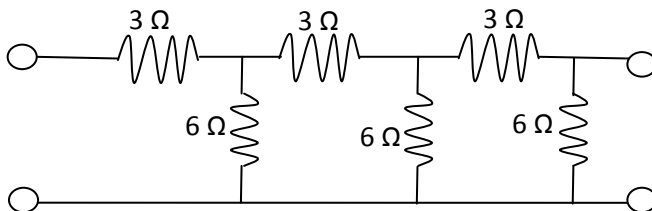- (b) For an RC series circuit, a sinusoidal voltage  $v(t) = V_m \sin \omega t$  is applied at  $t = 0$ . Find the expression for transient current.

- 8 (a) Determine Y-parameters of the network shown below.



- (b) The Z-parameters of a two port network are  $Z_{11} = 15\Omega$ ,  $Z_{22} = 24\Omega$ ,  $Z_{12} = Z_{21} = 6\Omega$ . Determine ABCD parameters.

\*\*\*\*\*