

**R07**

Code: R7100406

B.Tech I Year (R07) Supplementary Examinations December/January 2015/2016

**NETWORK ANALYSIS**

(Common to ECEM EIE, E.Con.E, ECC & CSS)

(For 2008 regular admitted batch only)

Time: 3 hours


Max. Marks: 80

Answer any FIVE questions


All questions carry equal marks

\*\*\*\*\*

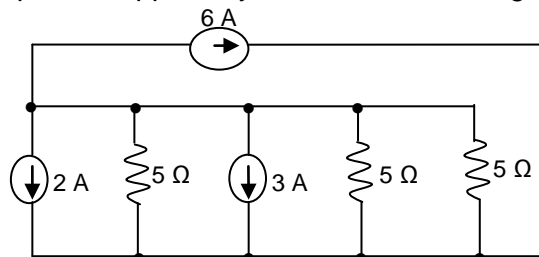
- 1 (a) If  $R_1$ ,  $R_2$ ,  $R_3$  are resistances of different branches of a star connected network. Find the equivalent branch resistances of the above network when converted into a delta network.
- (b) (i) Compute the power supplied by each source in the given circuit.



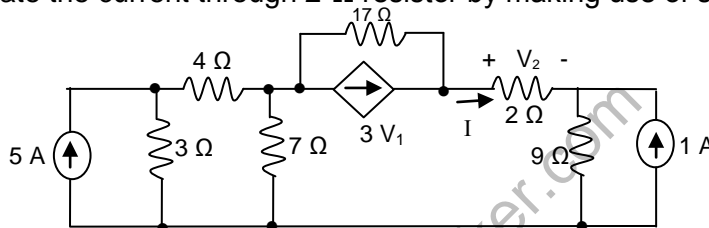- (ii) Calculate the current through  $2\Omega$  resistor by making use of source transformation.




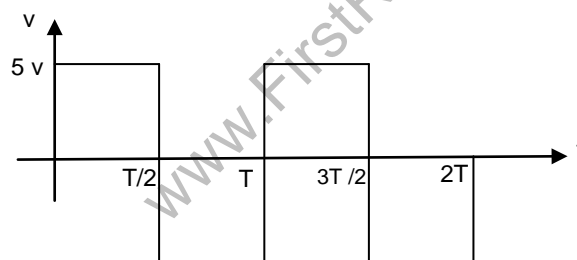- 2 (a) (i) Find average, RMS and form factor for the following wave form.



- (ii) If  $L_1$ ,  $L_2$  are self inductance of two inductors. Let  $M$  be the mutual inductance of the coils and  $K$  be the coefficient of coupling between them. Derive the relation between  $L_1$ ,  $L_2$  and  $M$  when these two coils are magnetically coupled.

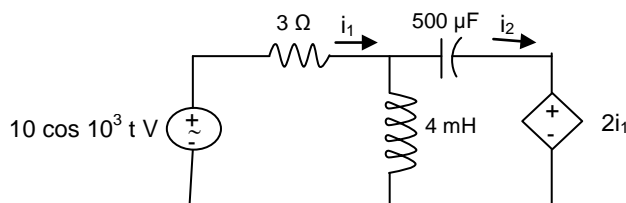- (b) Obtain expression for the time-domain currents  $i_1$  and  $i_2$  in the given circuit.




Contd. in page 2

**R07**


Code: R7100406

- 3 (a) (i) A series RLC resonant circuit composed of a  $10\ \Omega$  resistance a  $200\ \text{nF}$  capacitance, and a  $2\text{-mH}$  inductance. Calculate resonant frequency in radians, band width and also quality factor.  
(ii) A balanced three-phase three wire system has a star connected load. Each phase contain three loads in parallel they are  $-j100\ \Omega$ ,  $100\ \Omega$  and  $50+j50\ \Omega$ . Assume positive phase sequence  $V_{ab} = 400\ \text{V}$ . Find the total power drawn by the load.
- (b) In three-phase Y-Y connection derive the relationship between line and phase voltage and current with necessary phasor diagram.

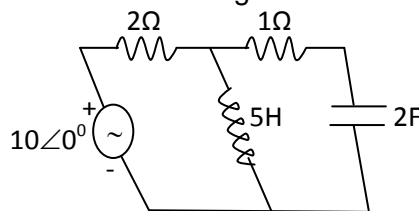
- 4 (a) (i) Find the dual network for the given circuit.



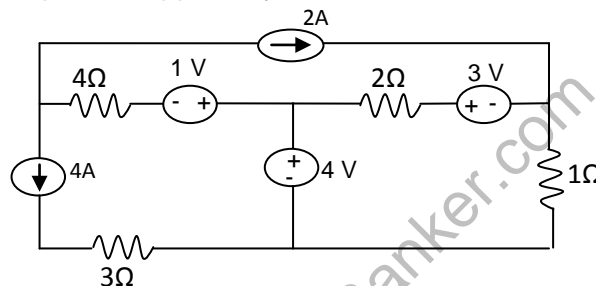- (ii) Explain the concept of cutset matrix with the help of simple planar network.  
(b) Determine the power supplied by  $2\text{A}$  source in the circuit using nodal analysis



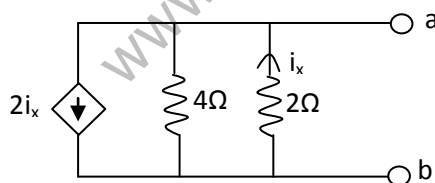- 5 (a) State and explain superposition theorem.  
(b) State and explain millimans theorem.  
(c) Find the thevinens equivalent for the given circuit.




Contd. in page 3

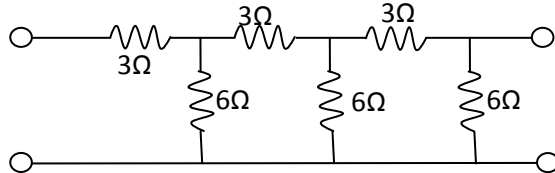**R07**

Code: R7100406


- 6 (a) Determine the ABCD parameters for the given circuit.



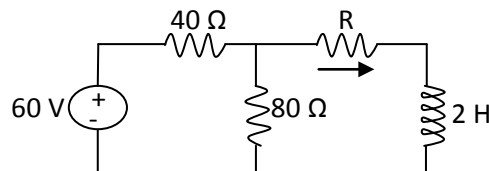
- (b) Derive the following relation of interconnected networks.

$$[Y] = [Y_a] + [Y_b]$$

- 7 (a) For the given circuit find the value of  $R$  for which energy stored in inductor will be 1J.



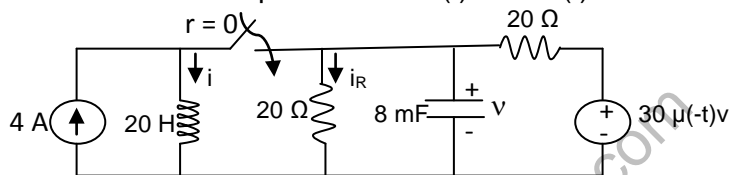- (b) In the circuit find the expressions for  $i(t)$  and  $i_R(t)$  for  $t > 0$ .



- 8 (a) Compare LP, HP, BP filter characteristics.  
(b) A filter section is required to have nominal impedance of  $600\Omega$ , a cut-off frequency of 5 KHz and frequency of infinite attenuation at 5.50 kHz. Design an appropriate m-derived T-section.

\*\*\*\*\*