

B.Tech I Year (R13) Supplementary Examinations December/January 2015/2016

ELECTRICAL CIRCUITS

(Electrical and Electronics Engineering)


Time: 3 hours

Max. Marks: 70

PART – A
(Compulsory Question)

1 Answer the following: (10 X 02 = 20 Marks)

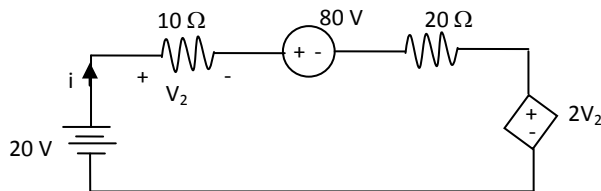- Explain the properties of series and parallel magnetic circuits.
- State how AC is supplied to DC.
- Explain measurement of reactive volt-ampere method and prove that: $W_r = \sqrt{3}(W_1 - W_2)$.
- Find the current 'I'.




- Explain line spectra and phase spectra in Fourier transforms.
- What are the properties of Fourier series and Fourier transforms?
- Explain parallel connection of two – port networks.
- The impedance function of a parallel networks has pole located at $-3 \pm j4$ rad/sec. If the value of $L = 1H$. Determine 'R'.
- Explain properties of Compensation and Tellegen's theorem.
- The number of turns on a coil having time constant of are doubled. The new time constant will be -----.

PART – B
(Answer all five units, 5 X 10 = 50 Marks)

UNIT – I

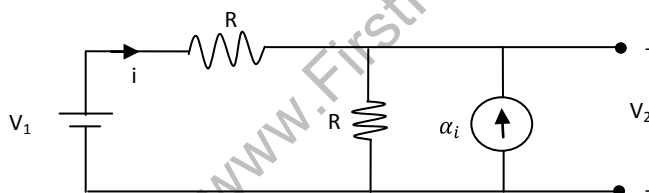
- 2 (a) Consider the circuit as shown in figure below which has the current-dependent current source. Also find the value of $\frac{V_2}{V_1}$.



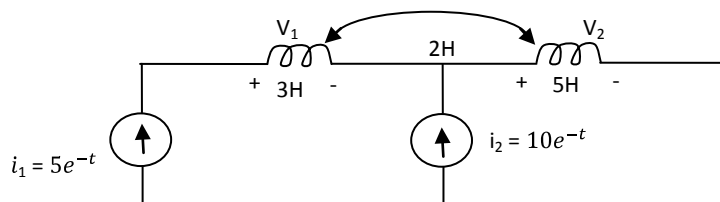- (b) What are the energy consideration in coupled circuits.

OR

- 3 (a) Find the instantaneous voltages V_1 and V_2 in the coupled inductance in the circuit.



- (b) Explain B-H curve and Hysteresis loop for magnetic material.


Contd. in page 2

UNIT – II


- 4 (a) A 440/254 volts, 3-phase, 4-core supplies an unbalanced load represented by the following impedances in ohms connected between R, Y, B and neutral $16+j12$, $14-j21$ and 25 . The phase sequence RYB. Calculate the current in each conductor of the cable and the reading on each of the three wattmeter's connected in each line and neutral.
- (b) What are the advantages of sinusoidal quantities over the other quantities?

OR

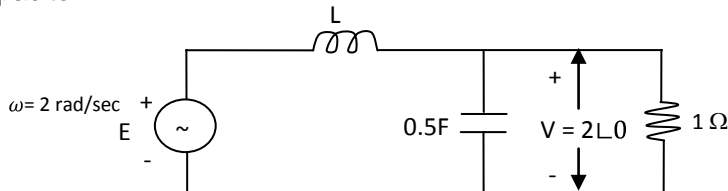- 5 (a) For the circuit shown below, how much the voltage across the inductor leads the voltage across the capacitor?




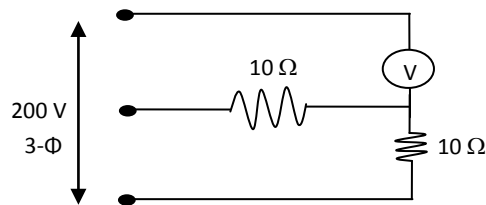- (b) A voltmeter with a resistance of 10 kW is connected as shown in figure below. Find the reading on the voltmeter. (i) In the condition shown. (ii) When the voltmeter shunted by a 5 kW resistor.




UNIT – III

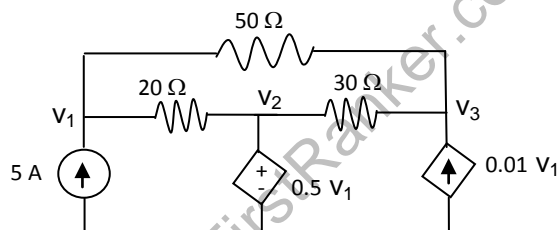- 6 (a) Explain admittance locus diagrams.
- (b) The following network use Nodal analysis to determine V_1 , V_2 and V_3 .



OR

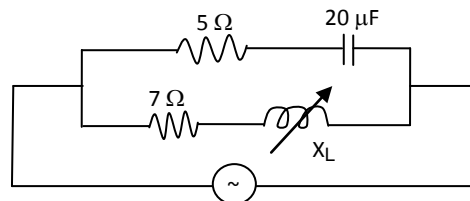- 7 (a) Explain properties of Cut set and Tie set and incident matrix.
- (b) The locus of the admittance locus shown in figure below. Determine the variable inductance values, so that the phase angle between the supply voltage and supply current is zero. Assume $\omega = 5000\text{ rad/sec}$.




Contd. in page 3

Code: 13A02101

R13

UNIT – IV

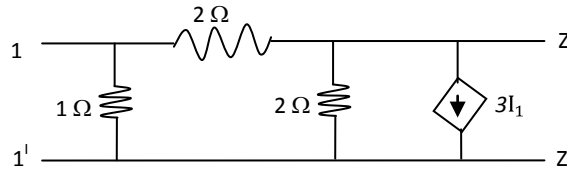
- 8 (a) Obtain the z-parameters for the following figure.



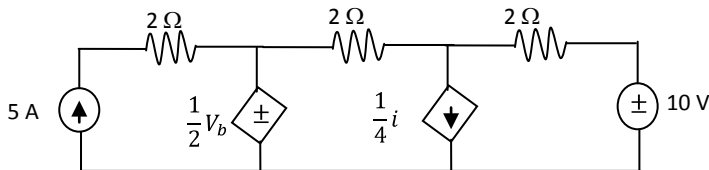- (b) State and explain maximum power transfer theorem with a circuit excited by A.C source.

OR

- 9 (a) Find the ' I_n ' in the circuit using Norton's theorem.




- (b) The following equations given the voltages V_1 and V_2 at the ports of a two – port networks:

$$V_1 = 5I_1 + 2I_2, \quad V_2 = 2I_1 - I_2$$

A load resistor of 3Ω is connected across port-2, calculate the input impedance.

UNIT – V

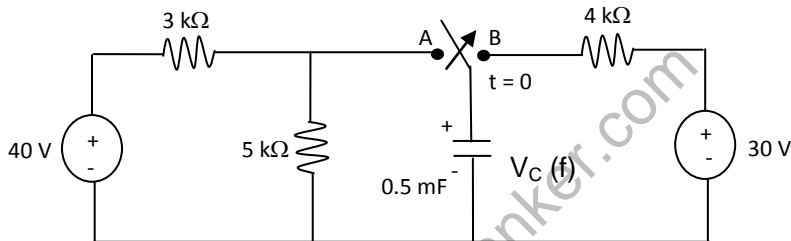- 10 For the circuit shown below, a switch has been in position A for a long time at $t = 0$, switch is moved to B then the capacitor voltage $V_C(t)$ for $t > 0$ is.



OR

- 11 (a) Derive the transient response in RLC circuit with sinusoidal excitation.
(b) Determine the relative frequency distribution of a single rectangular pulse of amplitude A and duration T.

