

Code: 9A02702

B.Tech IV Year I Semester (R09) Regular & Supplementary Examinations December 2015

FUNDAMENTALS OF HVDC & FACTS DEVICES

(Electrical & Electronics Engineering)

Time: 3 hours

Max. Marks: 70

Answer any FIVE questions
All questions carry equal marks

- 1 Explain in detail about different types of HVDC links available with the help of neat sketches.
- 2 (a) Explain the constant extinction angle control with a neat block diagram.
(b) Explain clearly the procedure for start up of a DC link.
- 3 (a) Discuss how shunt capacitors can be used to meet reactive power requirement of a converter.
(b) Discuss about characteristic and non-characteristic harmonics generated in HVDC systems.
- 4 (a) Derive the mathematical model of a HVDC converter.
(b) Explain the sequential method for AC-DC power flow.
- 5 Explain the basic types of the FACTS controllers and their applications.
- 6 Explain how the shunt compensation is useful in prevention of voltage instability and improvement of transient stability.
- 7 Explain the basic control schemes for GSC, TSSC and TCSC using block diagrams.
- 8 (a) Draw and explain the overall control structure of UPFC.
(b) Explain the basic control scheme for P and Q control by UPFC.
