

Code: R7210406

R07

B.Tech II Year I Semester (R07) Supplementary Examinations December 2015


ELECTRONIC CIRCUIT ANALYSIS
(Electronics & Communication Engineering)
(For 2008 regular admitted batch only)

Time: 3 hours

Max. Marks: 80

Answer any FIVE questions
All questions carry equal marks

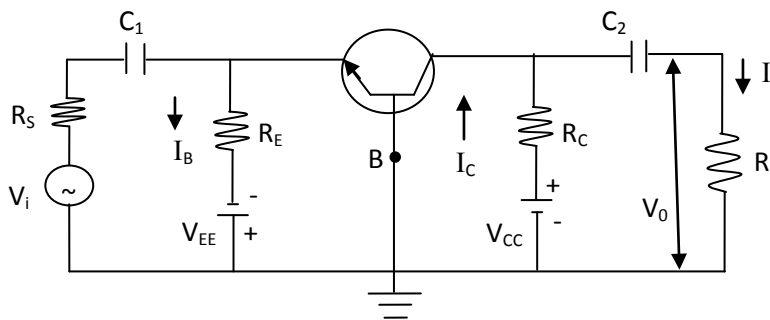- 1 (a) Explain the principle of operation of basic CE amplifier circuit. Give important characteristics of CE amplifier.
- (b) Calculate A_i , R_i , A_v and R_o for C-B amplifier shown below, with $R_L = 5 \text{ k}\Omega$, $R_S = 500 \text{ }\Omega$, $h_{fe} = 50$; $h_{ie} = 1 \text{ k}\Omega$, $h_{oe} = 50 \text{ k}\Omega$ and $R_E = 10 \text{ k}\Omega$ and $R_e = 10 \text{ k}\Omega$.



- 2 (a) When two-stage of identical amplifiers are cascaded, obtain the expressions for overall voltage gain, current gain and power gain.
- (b) For a given transistor (BJT) $H_{fe} = 100$, $f_B = 5 \text{ kHz}$. Determine the bandwidth of the transistor. If the lower cut-off frequency $f_1 = 100 \text{ MHz}$ and upper cut off frequency $f_2 = 100 \text{ kHz}$, then determine the mid-band frequency f_0 of the amplifier circuit.
- 3 (a) Draw the small-signal equivalent circuit for an emitter-follower stage at high frequencies. Find its value of input admittance.
- (b) Given a germanium p-n-p transistor whose base width is 10^{-4} cm . At room temperature and for a DC emitter current of 2 mA . Find: (i) Emitter diffusion capacitance. (ii) f_T (Assume diffusion constant as $47 \text{ cm}^2/\text{sec}$). What is the use of calculating noise figure?
- 4 (a) Explain why a power amplifier is always preceded by a voltage amplifier.
- (b) Explain the phenomenon of 'crossover distortion' that pops up in complementary symmetry push-pull amplifier circuit for class-B operation. Explain with necessary diagrams, how 'trickle bias' overcome the above problem.
- 5 (a) Draw a simple BJT tuned amplifier circuit and its ideal response characteristics.
- (b) Explain the principle of stagger tuning technique of transformer-coupled amplifier that is used to obtain band pass filter characteristics with pass band of 10 kHz with all necessary diagrams for illustration.
- 6 Explain in detail the effect of cascading tuned amplifiers and hence derive the expression for bandwidth of n-stage amplifier. Also draw the frequency response and explain what happens as the number of stages increases.
- 7 (a) Draw the circuit of a series regulator circuit to stabilize the DC output voltage and explain the design methodology.
- (b) Give the circuit of a short circuit overload protection that is to be provided in a voltage regulator circuit and explain its working.
- 8 (a) Draw the circuit for 7805 voltage regulator along with unregulated power supply and explain its working.
- (b) Draw the circuit diagrams of voltage doubler and voltage tripler circuits and explain their working. Explain in detail about Shannon Coding theorem.