

R09/SS

Code: 9A02305

B.Tech II Year I Semester (R09/R13) Regular & Supplementary Examinations December 2015

ELECTRICAL CIRCUITS


(Common to EEE, EIE, E.Con.E, ECE & ECC)

Time: 3 hours


Max. Marks: 70

Answer any FIVE questions
All questions carry equal marks

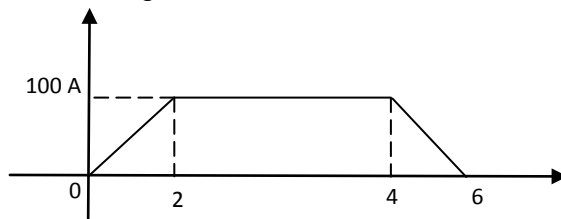- 1 (a) What is the difference between an ideal source and a practical source? Draw the relevant characteristics of the above sources.
- (b) A current wave form flowing through an inductor of 1mH is shown below. Obtain and sketch the waveform of the voltage across the inductor.



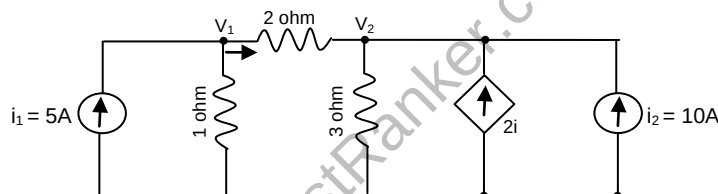- 2 (a) Explain the node analysis used in the circuit analysis.
- (b) For the network shown below figure, determine the node voltages V_1 and V_2 . Determine the power dissipated in each resistance.




- 3 (a) Explain concept of power and power factor of an RL circuit.
- (b) Consider the RL series circuit with an impedance angle of 50 degrees at a frequency of 60 Hz at what frequency the magnitude of the impedance will be twice the magnitude of the impedance at 60 Hz.
- 4 (a) Write the properties and applications of parallel resonant circuit.
- (b) A coil is connected in series with a variable capacitor across $V(t) = 1000t$. The capacitor is varied and the current is maximum when $C = 10$ micro farads. When $C = 12.5$ micro farads the current is 0.707 times the maximum value. Find L, R, and Q of the coil.
- 5 (a) Derive the expression for equivalent inductance of two coils connecting in series opposing.
- (b) An air cored solenoid has a length of 80 cm and a diameter of 2 cm. Calculate its inductance if it has 800 turns. Also, calculate the energy stored in the inductor if the current rises from 0 to 10 A. Calculate self induced emf in the solenoid.

Contd. in page 2


R09/SS

Code: 9A02305

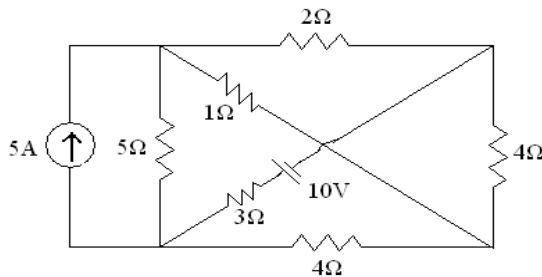- 6 Using nodal analysis find current through all the elements in the circuit shown below and also find power dissipated by all the resistors.



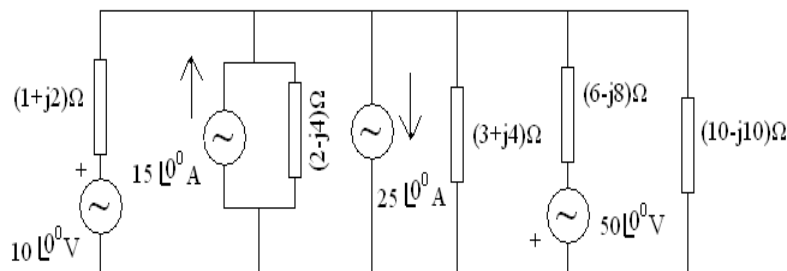- 7 (a) Find the condition for maximum power transfer to the load for A.C network, when load impedance is variable.
(b) Determine current through $(10-j10)\Omega$ impedance using Milliman's theorem.



- 8 (a) State and explain superposition theorem.
(b) Prove Tellegen's theorem for the network shown below figure.

