

B.Tech II Year I Semester (R13) Regular & Supplementary Examinations December 2015

NETWORK ANALYSIS

(Electronics and Communication Engineering)


Time: 3 hours

Max. Marks: 70

PART – A
(Compulsory Question)

1 Answer the following: (10 X 02 = 20 Marks)

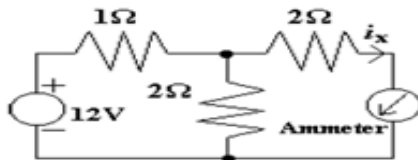(a) The value of i_x shown in following figure is:-----




- Define Tree and Co-Tree.
- Write the limitations of superposition theorem.
- A network N is to be connected to load of 500 ohms. If the Thevenin's equivalent voltage and Norton's equivalent current of N are 5 volts and 10mA respectively, calculate the current through the load.
- The Q-factor of a parallel resonance circuit consisting of an inductance of value 1mH, capacitance of value 10^{-5} F and a resistance of 100 ohms is.
- Define resonant frequency.
- Define Reciprocity theorem.
- Explain maximum power transfer theorem.
- What do you mean by the state? What are state variables?
- Write the applications of different types of filters?

PART – B

(Answer all five units, 5 X 10 = 50 Marks)


UNIT – I

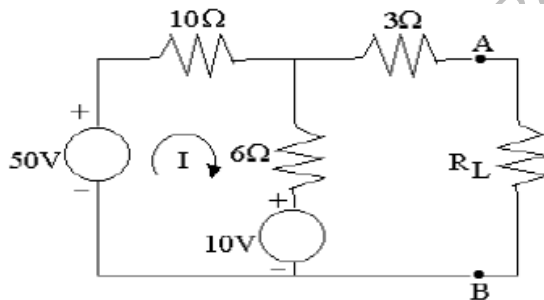2 Obtain the Thevenin's equivalent of the network shown in figure below. Then draw the Norton's equivalent network by source transformation.



OR

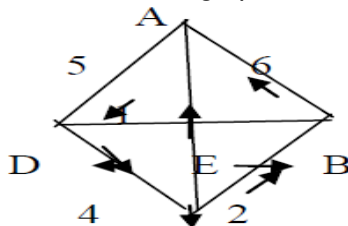3 (a) For the directed graph shown bellow obtain the cut set matrix.




(b) State and prove superposition theorem and Millman's theorem.

Contd. in page 2

UNIT – II

- 4 (a) An inductive coil, having resistance of $8\ \Omega$ and inductance of 80 mH , is connected in series with a capacitance of $100\ \mu\text{F}$ across 150 V , 50 Hz supply. Calculate: (i) The current. (ii) The power factor. (iii) The voltages drop in the coil and capacitance respectively.
- (b) The power consumed in the inductive load as shown in figure below is 2.5 kW at 0.71 lagging power factor (pf). The input voltage is 230 V , 50 Hz . Find the value of the capacitor C , such that the resultant power factor of the input current is 0.866 lagging.

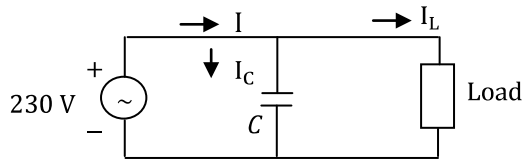

OR

- 5 (a) Derive RMS value of alternating quantity from fundamentals
- (b) A 50 Hz sinusoidal voltage applied to a single phase circuit has its RMS value of 200 V , its value at $t = 0$ is 28.3 volts positive. The current drawn by the circuit is 5 A r.m.s and lags behind the voltage by one sixth of a cycle. Write the expressions for instantaneous values of voltage and current.

UNIT – III


- 6 (a) Derive the expressions of quality factor using the general definition and show that greater the quality smaller the band width, using current Vs angular frequency plot for various values.
- (b) Consider a series resonance circuit consisting of a 10 ohms resistance, a 2mH inductance and a 200nF capacitance. Determine the maximum energy stored, the energy dissipated per cycle of the circuit.

OR


- 7 (a) Define coefficient of magnetic coupling. Derive the expression for coefficient of magnetic coupling.
- (b) Write the properties of ideal transformer and analyze ideal transformer.

UNIT – IV

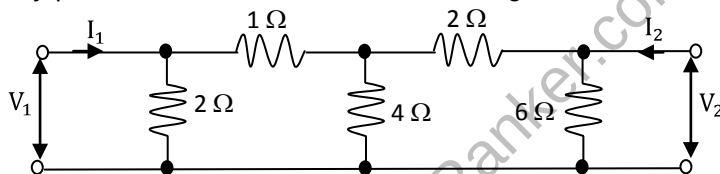- 8 (a) Find the y-parameters for the network shown in figure below.




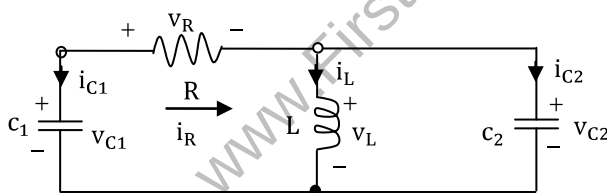- (b) Form the state matrix equation for the network shown in figure bellow.



OR

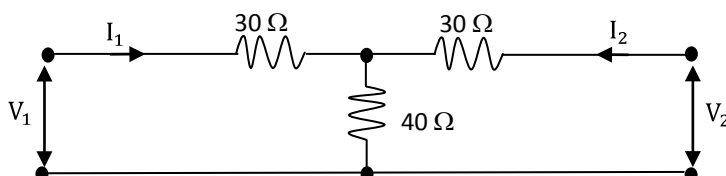- 9 For the symmetrical 2-port network shown in figure below, find the z-and ABCD-parameters.



UNIT – V

- 10 (a) State and explain the characteristics of passive filter
- (b) Design a T-section constant K-high pass filter having cut-off frequency of 10 kHz and design impedance $R_0 = 600\ \Omega$. Find its characteristic impedance and phase constant at 25 kHz .

OR

- 11 (a) Explain briefly about M-derived high pass filter.
- (b) Design an M-derived high pass filter having a design impedance of $600\ \Omega$, cut off frequency of 5 kHz and $m = 0.35$. Also determine the frequency of infinite attenuation.