

Code: 9A02401

R09

B.Tech II Year II Semester (R09) Supplementary Examinations December/January 2015/2016

PRINCIPLES OF ELECTRICAL ENGINEERING

(Common to EIE, E.Con.E, ECE & ECC)


Time: 3 hours

Max. Marks: 70

Answer any FIVE questions

All questions carry equal marks

- 1 (a) Derive the expression for current when a dc voltage V is applied suddenly (i.e. at time = 0) by closing a switch in a series R-C circuit
- (b) In a series R-L circuit, the application of a direct voltage results a steady state current of 0.6321 in 1 second. 'I' being the final steady state value of the current. However, after the current has reached its final value, a sudden short circuit is applied against the source. What would be the value of the current after one second?
- 2 (a) Define and obtain Impedance parameters by taking any one example.
- (b) Obtain 'Y' – parameters for the given network shown below.

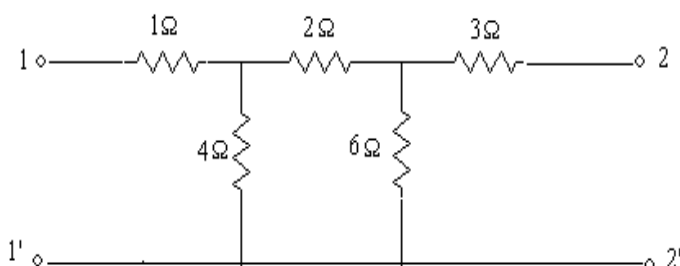

- 3 Design an m-derived low pass filter having design resistance $R_0 = 500 \Omega$, cut-off frequency $f_c = 1500$ Hz and infinite attenuation frequency $f_\alpha = 2000$ Hz.
- 4 What is an attenuator? Derive the design equations for Bridged T-type attenuator.
- 5 (a) Explain the principle of operation of DC generator.
- (b) A 6 – pole, Lap wound armature has 840 conductors and flux per pole of 0.018 Wb. Calculate the emf generated when the machine is running at 600 rpm.
- 6 A 220 V, shunt motor takes 4 A on no-load. The resistance of the armature including the brushes is 0.1 ohm and the field current is 1 A. Estimate the output and the efficiency when the input current is 50 A.
- 7 (a) Discuss the constructional details of a shell type transformer.
- (b) A 5 kVA, 200/400 V, 50 Hz single phase transformer gave the following results:
OC test: 220 V, 0.7 A, 60 W on LV side
SC test: 22 V, 10 A, 120 W on HV side
Determine the efficiency of transformer at full load having a load power factor of 0.8 lagging.
- 8 (a) Explain the principle of operation of Synchros.
- (b) Explain the characteristics of Stepper motor.