

Code: 9A02406

B.Tech II Year II Semester (R09) Supplementary Examinations December/January 2015/2016

**NETWORK THEORY**

(Electrical & Electronics Engineering)

Time: 3 hours


Max. Marks: 70

Answer any FIVE questions


All questions carry equal marks

\*\*\*\*\*


- 1 (a) Explain the measurement of power in a balanced 3-phase system using a single watt meter.  
(b) Three inductive coils, each with a resistance of  $13 \Omega$  and an inductance of  $0.07 \text{ H}$  are connected in delta to three phase  $440 \text{ V}$ ,  $50 \text{ Hz}$  supply. Calculate: (i) Phase current and line current. (ii) Total power absorbed.
- 2 A 3- $\Phi$   $500 \text{ V}$  motor load has a power factor of  $0.4$ . Two wattmeters are connected to measure the input. They show the input to be  $30 \text{ kW}$ . Find the reading of each instrument. Derive the formulae used.
- 3 (a) Derive the expression for current when a dc voltage  $V$  is applied suddenly (i.e. at time  $= 0$ ) by closing a switch in a series R-L circuit.  
(b) A direct voltage of  $200 \text{ V}$  is suddenly applied to a series L-R circuit having  $R = 20 \Omega$  and inductance  $0.2 \text{ H}$ . Determine the voltage drop across the inductor at the instant of switching on and at  $0.02 \text{ sec}$ . later
- 4 In the following circuit shown below, switch 'K' is closed at time  $t = 0$ . Obtain expression for the current  $i(t)$ .

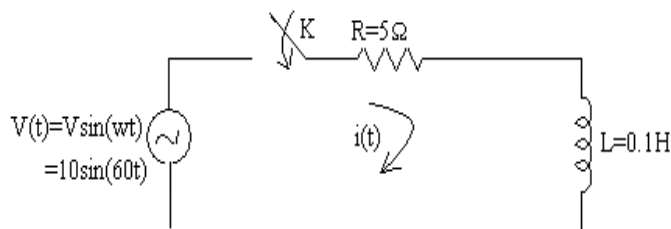

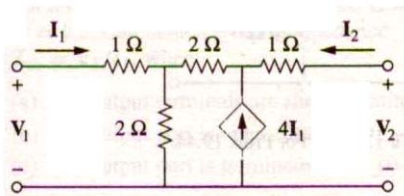- 5 Obtain the h-parameters for the two port of figure given below:



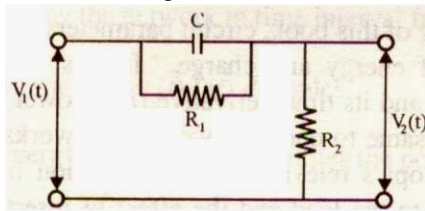- 6 Find the voltage transfer function of the network shown below:



- 7 Express the Fourier series  $f(t) = 10 + \sum_{n=1}^{\infty} \frac{4}{n^{2+1}} \cos 10nt + \frac{1}{n^3} \sin 10nt$  in a sine and angle form.
- 8 Calculate the fraction of the total energy dissipated by a  $1 \Omega$  resistor in the frequency band  $-10 < \omega < 10$  rad/sec when the voltage across it is  $v(t) = e^{-2t} u(t)$

\*\*\*\*\*