

B.Tech II Year II Semester (R09) Supplementary Examinations December/January 2015/2016

**ELECTRONIC CIRCUIT ANALYSIS**

(Common to EIE, E.Con.E & ECE)


Time: 3 hours

Max. Marks: 70

Answer any FIVE questions  
All questions carry equal marks

\*\*\*\*\*

- 1 (a) Draw the hybrid model of CB & CC configurations. Explain.
- (b) The circuit shown has parameters  $V^+ = 5\text{ V}$ ,  $V^- = 5\text{ V}$ ,  $R_E = 4\text{ k}$ ,  $R_C = 4\text{ k}$ ,  $R_B = 100\text{ k}$  and  $R_S = 0.5\text{ k}$ . The transistor parameters are  $\beta = 120$ ,  $V_{BE(on)} = 0.7\text{ V}$ , and  $V_A = 80\text{ V}$ .
  - (i) Determine the input resistance seen by the signal source.
  - (ii) Find the small-signal voltage gain.

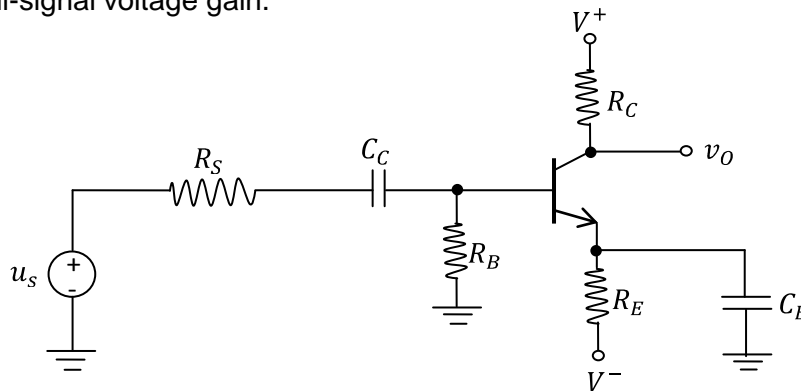

- 2 (a) Compare the direct and transformer coupled amplifiers.
- (b) What is CE-CC amplifier? Obtain its voltage gain.
- 3 (a) What is the importance of gain bandwidth product? Explain.
- (b) Obtain the hybrid- $\Pi$  parameters in terms of h-parameters.
- 4 (a) What are the applications of MOSFET amplifiers? Explain.
- (b) Compare CS and CG MOSFET amplifiers.
- 5 (a) How bandwidth increases and distortion decreases due to negative feedback? Explain.
- (b) Show that the stabilization gain of negative feedback amplifier is  $\left| \frac{dA_f}{A_f} \right| = \frac{\left| \frac{dA}{A} \right|}{|1 + A\beta|}$ .
- 6 (a) Where crystal oscillator is used? Explain with the equivalent circuit.
- (b) Draw the circuit diagram of Colpitts oscillator. Explain its operation. Show that the frequency of oscillations is  $f = \frac{1}{2\pi\sqrt{LC_{eq}}}$ , where  $C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$ .
- 7 (a) Explain about the class-B complementary and symmetry power amplifier and obtain its efficiency.
- (b) What are the advantages and disadvantages of class-B complementary and symmetry power amplifier? Explain.
- 8 (a) Explain the concept of stagger tuned with frequency response.
- (b) Explain about effect of cascading single and double tuned amplifiers on bandwidth.