

R07**Code: R7310204**

B.Tech III Year I Semester (R07) Supplementary Examinations December 2015

POWER ELECTRONICS

(Common to EEE and E.Con.E)

(For 2008 regular admitted batch only)

Time: 3 hours

Max Marks: 80

Answer any FIVE questions

All questions carry equal marks

- 1 (a) Distinguish between power BJT and Power MOSFET.
(b) With the help of neat structural diagram and suitable waveforms, explain the operation of IGBT.
- 2 (a) What is the necessity of connecting SCRs in series?
(b) What are the problems associated with series connection of SCRs? How are they eliminated?
- 3 (a) Explain the operation of 1-phase half controlled bridge converter with R-load and associated waveforms.
(b) Derive the expression for average load voltage for $\alpha = 30^\circ$.
- 4 A single phase full-wave mid-point converter with freewheeling diode is supplied from a 120 V, 50 Hz supply with a source inductance of 0.33mH. Assuming the load-current is continuous at 4 A. Find the overlap angles for:
(a) Transfer of current from a conducting thyristor to the commutating diode.
(b) From the commutating diode to a thyristor when the firing angle is 45° .
- 5 (a) Describe the operation of three pulse converter with R-load and draw associate waveforms.
(b) Derive the voltage and RMS current relationships for three pulse converter with R-load.
- 6 Describe the operation of single phase half-wave ac voltage regulator with the help of voltage and current waveforms. Also, derive the expression for average value of output voltage.
A single-phase half-wave a.c voltage controller feeds power to resistive load of $6\ \Omega$ from 230 V, 50 Hz source. The firing angle of SCR is $\pi/2$. Calculate:
(i) The RMS value of output voltage.
(ii) The input power factor.
(iii) The average input current.
- 7 (a) Derive an expression for output power for type D chopper.
(b) Explain in detail the principle operation of the four quadrant chopper.
- 8 (a) Write the comparison between voltage sourced inverter and current sourced inverter.
(b) A capacitor commutated 1-phase bridge inverter is operated at 50 Hz with load resistance of $5\ \Omega$. Thyristor turn off time is $62\ \mu\text{s}$. Determine: (i) Commutating capacitor C for successful commutation of SCR. (ii) Load current I_L .
