

R09**Code: 9A10504**

B.Tech III Year I Semester (R09) Supplementary Examinations December 2015

LINEAR & DIGITAL IC APPLICATIONS

(Common to E.Con.E, EIE and ECC)

Time: 3 hours

Max Marks: 70

Answer any FIVE questions
All questions carry equal marks

- 1 (a) Draw the block diagram of a 741 Op amp and discuss its features.
(b) Explain slew rate, CMRR, PSRR and drift.
- 2 (a) Explain the working of an instrumentation amplifier using Op amps.
(b) How does an Op amp work as an integrator and differentiator?
- 3 (a) Draw the characteristic waveforms and explain the working of a Schmitt trigger.
(b) Write short notes on FM and FSK.
- 4 (a) Explain the dynamic electrical behavior of CMOS.
(b) Discuss different logic families with respect to their features.
- 5 (a) Compare 74XX and CMOS 40XX.
(b) Write short notes on low voltage CMOS logic and interfacing.
- 6 (a) Write about libraries and packages used in VHDL.
(b) With an example, explain data flow design elements.
- 7 (a) Write short notes on Mux, De Mux and Code converters.
(b) Explain the action of parity circuits and comparators.
- 8 (a) Draw the VHDL model of a shift register and explain.
(b) Discuss the impediments to synchronous design.
