

B.Tech III Year I Semester (R13) Regular Examinations December 2015

LINEAR & DIGITAL IC APPLICATIONS

(Electronics and Instrumentation Engineering)

Time: 3 hours

Max. Marks: 70

PART – A
(Compulsory Question)

- 1 Answer the following: (10 X 02 = 20 Marks)
- (a) Give the classification of ICs.
 - (b) What is the significance of an AC amplifier?
 - (c) Define comparator.
 - (d) Draw the block schematic of the PLL.
 - (e) Draw the basic CMOS inverter circuit.
 - (f) List the characteristics of Emitter Coupled Logic (ECL).
 - (g) List the features of VHDL.
 - (h) What are the different ways to specify a time delay in a VHDL code?
 - (i) Give the importance of three state devices.
 - (j) Define clock skew.

PART – B
(Answer all five units, 5 X 10 = 50 Marks)**UNIT – I**

- 2 (a) Define the following:
(i) CMRR. (ii) PSRR. (iii) Slew rate.
- (b) Draw and explain the operation of current to voltage converter

OR

- 3 (a) Design a differentiator to differentiate an input signal that varies in frequency from 10 Hz to about 1 kHz.
- (b) Discuss the different types of linear IC packages.

UNIT – II

- 4 (a) Explain any two applications of PLL.
- (b) Draw and explain the operation of Antilog amplifier.

OR

- 5 (a) A Schmitt trigger with the upper threshold level $V_{UT} = 0$ V and hysteresis width $V_H = 0.2$ V converts a 1 kHz sine wave of amplitude $4V_{PP}$ into a square wave. Calculate the time duration of the negative and positive portion of the output waveform.
- (b) With a neat sketch explain the operation of triangular waveform generator.

UNIT – III

- 6 (a) Give the comparison of logic families.
- (b) Explain how to estimate sinking current for low output and sourcing current for high output of CMOS gate.

OR

- 7 (a) Discuss in brief about CMOS/TTL interfacing.
- (b) Explain the following terms with reference to CMOS logic:
(i) Logic levels. (ii) Power supply rails

UNIT – IV

- 8 Explain in detail about the steps involved in HDL-based design flow.

OR

- 9 (a) Explain with an example, the syntax and the function of the following VHDL statements:
(i) Case statement. (ii) Loop statement.
- (b) Write a brief note on simulation.

UNIT – V

- 10 Design a logic circuit of Binary to Gray code converter and write a data flow VHDL program.

OR

- 11 (a) Design a conversion circuit to convert a T flip-flop from D flip-flop.
- (b) Give the comparison between Moore and Mealy circuits.