

R07**Code: R7320206**

B.Tech III Year II Semester (R07) Supplementary Examinations December/January 2015/2016

VLSI DESIGN

(Common to EEE, E.Con.E and ECE)

(For 2008 regular admitted batch only)

Time: 3 hours

Max Marks: 80

Answer any FIVE questions
All questions carry equal marks

- 1 (a) What are the advantages of CMOS technology?
(b) Draw the flow chart for VLSI design flow and explain clearly about each step.
- 2 Draw the small signal AC characteristics of MOS transistor. And derive expression for g_m in different regions.
- 3 Draw CMOS inverter, its physical lay out with its stick diagram.
- 4 (a) What is a transmission gate? Explain clearly about it. Draw the symbols of transmission gate.
(b) Implement XOR gate using transmission gate.
- 5 (a) Write about switch logic.
(b) Implement 4:1 multiplexer using Switch logic and compare it with gate logic implementation?
- 6 (a) Discriminate between testing and simulation in IC designing.
(b) Implement the following function using PAL:
$$f_1 = \overline{ABC} + AB + BC + CA$$
$$f_2 = ABC + A\overline{B}C + \overline{A}BC$$
- 7 What is meant by simulation? Explain in detail about switch level and circuit level simulation?
- 8 (a) What is a Fault Model? Explain in detail about Stuck at Fault Model?
(b) Explain the terms Fault simulation, Fault coverage and Fault collapsing.
