

R09**Code: 9A04605**

B.Tech III Year II Semester (R09) Supplementary Examinations December/January 2015/2016

VLSI DESIGN

(Common to ECE, EIE and E.Con.E)

Time: 3 hours

Max Marks: 70

Answer any FIVE questions
All questions carry equal marks

- 1 (a) What is SOI process? Explain clearly about the advantages and disadvantages of it.
(b) Write about floating body voltage.
- 2 (a) Explain the Tunneling mechanism in MOS devices.
(b) How does the transistor characteristics are influenced by the temperature?
- 3 Design a layout diagram for two input NMOS NOR gate.
- 4 (a) Realize the logic function $[(AB)+(CD)]'$ using compound gates.
(b) Realize the logic function $x_1' + x_2' x_3'$ using compound gates.
- 5 (a) Write about switch logic and hence compare the properties of pass transistor and transmission gate used as switches in NMOS and CMOS respectively.
(b) Implement 8:1 multiplexers using CMOS switch logic.
- 6 (a) Explain about the designing of a chip with sea of gates (SOG).
(b) Write about FPGA.
- 7 What is meant by logic synthesis? Explain in detail the advantages and disadvantages of network restructuring in order to obtain logic optimization.
- 8 (a) Differentiate between chip level test techniques and system level techniques.
(b) Explain any one of the chip level and system level methods.
