

B.Tech II Year I Semester (R13) Supplementary Examinations June 2016

**ELECTRONIC DEVICES & CIRCUITS**

(Common to EEE, ECE & EIE)

Time: 3 hours

Max. Marks: 70

**PART – A**  
(Compulsory Question)

\*\*\*\*\*

- 1 Answer the following: (10 X 02 = 20 Marks)
- Define intrinsic semi conductor, write example.
  - What are the basic applications of conventional and Zener diode?
  - Write the formula for  $\beta$  in terms of  $\alpha$ , and in terms of  $\gamma$  of a NPN transistor.
  - For a transistor  $\alpha$  is 0.99, what is  $\beta$ ?
  - List out the types of biasing techniques.
  - Define thermal runaway.
  - Draw the h-parameter model of CE mode.
  - Write the typical values of  $h_{ie}$ ,  $h_{fe}$ ,  $h_{re}$  &  $h_{oe}$ .
  - Define thyristor family.
  - Draw the symbols of UJT and Tunnel diode.

**PART – B**

(Answer all five units, 5 X 10 = 50 Marks)

**UNIT – I**

- 2 (a) The leakage current through Germanium diode is  $I_o = 25 \mu A$ , if the forward bias of  $V_f = 0.2 V$ , Calculate the static resistance.
- (b) What are the various breakdown mechanisms? Explain one in detail.

**OR**

- 3 The Half wave rectifier circuit is supplied with a 230 V AC through 3:1 step down transformer with a resistive load of 10 K $\Omega$ , the diode forward resistance is 75  $\Omega$  and transformer secondary winding resistance 10  $\Omega$ . Calculate  $V_m$ ,  $I_m$ ,  $I_{av}$ ,  $V_{av}$  and  $P_{DC}$ .

**UNIT – II**

- 4 (a) Write the current components of PNP transistor and explain.
- (b) For a transistor the leakage current is 0.1  $\mu A$  in CB configuration, while it is 19  $\mu A$  when it is connected in CE configuration. Calculate  $\alpha$  and  $\beta$  of the same transistor.

**OR**

- 5 Draw and explain construction and operation of Enhancement mode MOSFET with its characteristics.

**UNIT – III**

- 6 Draw the BJT self bias circuit and derive equations for  $I_B$ ,  $I_C$  and  $V_{CE}$ .

**OR**

- 7 (a) In a fixed bias circuit a Si transistor with  $\beta = 100$  is used,  $V_{CC} = 6 V$ ,  $R_C = 3 K\Omega$ ,  $R_B = 530 K\Omega$ . Draw the DC load line, determine the Q point, What is the stability factor?
- (b) What are the advantages of self bias over other biasing techniques?

**UNIT – IV**

- 8 For a CE amplifier circuit  $R_S = 1 K\Omega$ ,  $R_1 = 50 K\Omega$ ,  $R_2 = 2 K\Omega$ ,  $R_C = 1 K\Omega$ ,  $R_L = 1.2 K\Omega$ . Construct small signal equivalent model and Calculate  $A_i$ ,  $A_v$ ,  $R_i$  and  $R_i'$ .

**OR**

- 9 (a) State and explain Millers theorem.
- (b) A Common Emitter amplifier with collector to Base bias having  $R_S = 10 K\Omega$ ,  $R_f = 200 K\Omega$  and  $R_C = 10 K\Omega$ . Calculate  $A_i$ ,  $R_i$ ,  $A_v$ . and  $R_i'$ .

**UNIT – V**

- 10 With neat diagrams, explain the construction and operation of SCR with its characteristics

**OR**

- 11 Draw and explain the construction and operation of UJT

\*\*\*\*\*