

B.Tech II Year I Semester (R13) Supplementary Examinations June 2016

**ELECTRICAL & ELECTRONICS ENGINEERING**

(Mechanical Engineering)

Time: 3 hours

Max. Marks: 70

Answer all questions  
All questions carry equal marks

\*\*\*\*\*

**PART – A**

**(Electrical Engineering)**

**UNIT – I**

- 1 (a) What is meant by residual magnetism, derive the expression for generated e.m.f in d.c shunt generator?  
(b) A shunt generator has a no-load voltage of 250 V when running at a speed of 800 rpm. The terminal voltage drops by 8% when the generator is delivering full load. If the resistances of the armature and the field windings are  $0.08 \Omega$  and  $92 \Omega$  respectively, compute the: (i) Output. (ii) Input torque of the generator at full load.

**OR**

- 2 (a) Explain the principle and operation of DC machine working as motor.  
(b) Discuss the characteristics of dc motors.

**UNIT – II**

- 3 (a) Obtain the equivalent circuit referred to primary side of single phase transformer.  
(b) The open circuit and short circuit tests on a 4-kVA, 200/400 V 50 Hz single phase transformer gave the following results:  
OC test on the LV side: 200 V, 1A, 100 W  
SC test with the LV side shorted: 15 V, 10A, 85W  
Determine the parameters of the equivalent circuit and draw the equivalent circuit referred to LV-side.

**OR**

- 4 (a) Explain the construction of a magnetic core of a transformer  
(b) A 10 KVA, 6600/220 V, 50 Hz transformer is rated at 2.5 V/turn of the winding coils. Assume the transformer to be ideal and calculate: (i) Step-up transformation ratio. (ii) Step-down transformation ratio. (iii) The total turns of high voltage and low voltage coils. (iv) The primary and secondary currents as a step-down transformer.

**UNIT – III**

- 5 (a) Explain the relationship between slip and rotor frequency.  
(b) Explain the torque slip characteristics of an induction motor for different values of rotor resistances.

**OR**

- 6 Explain the procedure for evaluating of voltage regulation by synchronous impedance method

**PART – B**

**(Electronics Engineering)**

**UNIT – I**

- 7 Explain about Zener diode and its characteristics and also explain how it works as a voltage regulator.

**OR**

- 8 Discuss about Diode switching characteristics.

**UNIT – II**

- 9 (a) A transistor has  $I_b = 100\mu A$  and  $I_c = 2mA$ . Find: (i)  $\beta$  of the transistor. (ii)  $\alpha$  of the transistor. (iii) Emitter current  $I_e$ . (iv) If  $I_b$  changes by  $+25\mu A$  and  $I_c$  changes by  $+0.6mA$ , find the new value of ' $\beta$ '.  
(b) Explain how a transistor can act as an amplifier

**OR**

- 10 (a) A FET has a drain current of 4mA. If  $I_{DSS} = 8mA$  and  $V_{GS\ off} = -6 V$ . Find values of  $V_{GS}$  and  $V_P$ .  
(b) Define  $\alpha_{dc}$  and  $\beta_{dc}$  of a transistor and derive the relation between them.

**UNIT – III**

- 11 Find out the 9's complement of following decimal numbers: (i) 459. (ii) 36. (iii) 1697.

**OR**

- 12 (a) Convert 3C, 104, 3A0 from hexadecimal to decimal  
(b) Why digital circuits are more frequently constructed with NAND or NOR gates than AND and OR gates? Explain.