

Code: 9A04402

B.Tech II Year II Semester (R09) Supplementary Examinations May/June 2016

ELECTRONIC CIRCUITS ANALYSIS

(Common to EIE, E.Con.E & ECE)

Time: 3 hours

Max. Marks: 70

Answer any FIVE questions
All questions carry equal marks

- 1 (a) Find the expressions of voltage, current gain, input and output resistances of CE, CB and CC amplifiers and compare them.
(b) Give wide classification of amplifiers based on various factors.
- 2 (a) Three amplifiers are connected in cascade. If the individual lower and higher 3dB frequencies are 20 Hz and 20 KHz, find the overall lower and higher 3 dB frequencies.
(b) What are various coupling schemes in amplifiers? Draw and explain the operation of a direct couple amplifier.
- 3 (a) What is unity gain bandwidth of a transistor and derive an expression for it?
(b) Derive the expression for voltage gain of a CE amplifier considering the effect of emitter bypass capacitor.
- 4 (a) Draw the circuit diagram of a common source amplifier and derive an expression for its gain.
(b) Draw the circuit of a CS stage with diode-connected PMOS load and derive expressions for its gain, input and output resistances.
- 5 (a) What is a negative feedback? Quantitatively discuss about its advantages and disadvantages.
(b) Draw the circuit of a base to emitter bias resistor circuit with $R_e = 0$, and perform the linear analysis using the concept of negative feedback.
- 6 (a) What is a Barkhausen criterion in oscillators? State and explain the three postulates of it.
(b) Derive the expression for frequency of oscillation and condition for sustained oscillations of a RC-phase shift oscillator.
- 7 (a) Draw the circuit diagram of a class A push-pull power amplifier and enumerate its advantages and disadvantages.
(b) Derive the expression for conversion efficiency of a class B power amplifier.
- 8 (a) Discuss about amplitude and frequency stability of tuned amplifiers.
(b) What is the concept of staggering? Draw and discuss the operation of tuned amplifier.
