

B.Tech I Year (R13) Supplementary Examinations June 2017

ELECTRICAL CIRCUITS

(Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 70

PART – A

(Compulsory Question)


- 1 Answer the following: (10 X 02 = 20 Marks)
 - (a) An energy source forces a constant current of 2 A for 10 sec to flow through a light bulb. If 2.3 kJ is given off in the form of light and heat energy. Calculate the voltage drop across the bulb.
 - (b) Derive the expression for the energy in the coupled circuit.
 - (c) For a sinusoidal waveform define form factor, average value and RMS value.
 - (d) Find the amplitude, phase, period and frequency of the sinusoid $V(t) = 12 \cos(50t + 10^\circ)$.
 - (e) Derive the expression for the resonant frequency for a series resonant circuit.
 - (f) Define graph, tree, cutset and Tieset with an example.
 - (g) State Thevenin and Nortons theorems.
 - (h) What are h-parameters? Explain them briefly with derivation.
 - (i) Determine the Laplace transform of each of the following functions:
 - (i) $u(t)$. (ii) $e^{-at}u(t), a \geq 0$.
 - (j) State the differentiation theorem of Fourier transform.

PART – B

(Answer all five units, 5 X 10 = 50 Marks)


UNIT - I

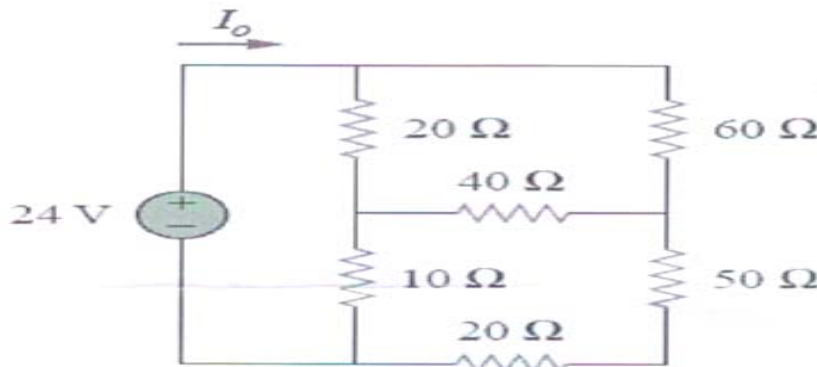- 2 Calculate I_0 for the circuit shown in figure below.



OR

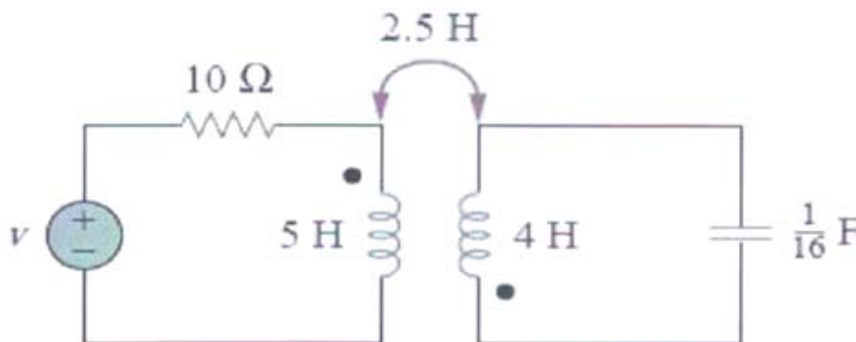
- 3 Consider the circuit shown in figure below. Determine the coupling coefficient calculate the energy stored in the coupled inductors at time $t = 1$ sec, if $V = 60 \cos(4t + 30^\circ)V$.



Contd. in page 2


UNIT - II

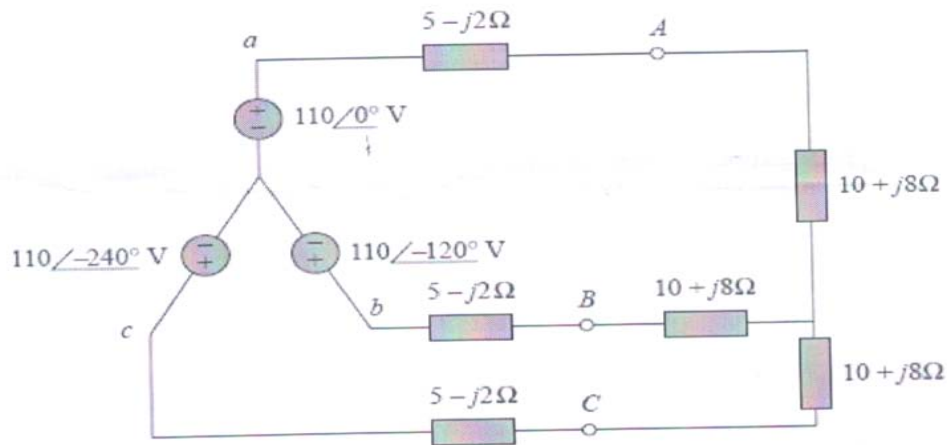- 4 Refer to the circuit shown in figure below. Calculate the average active power and reactive power at source and the load.




OR

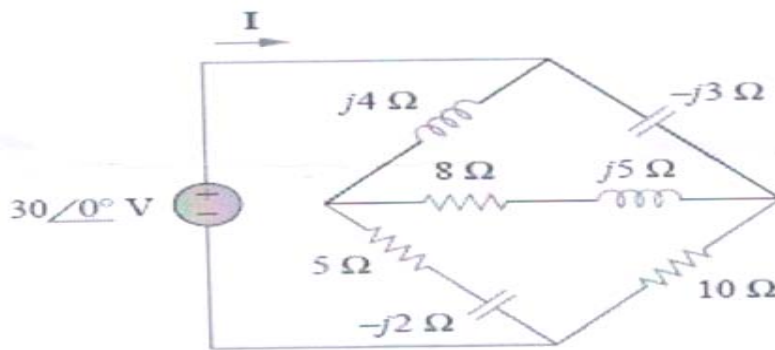- 5 Determine the current I for the circuit shown in figure below.




UNIT - III

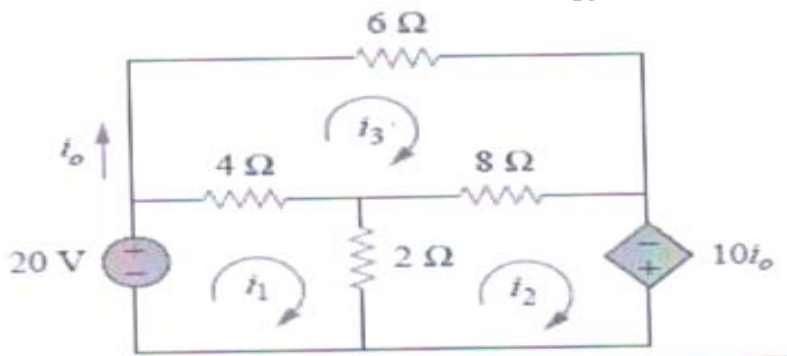- 6 Using Mesh Analysis find I_0 for the circuit shown in figure below.




OR

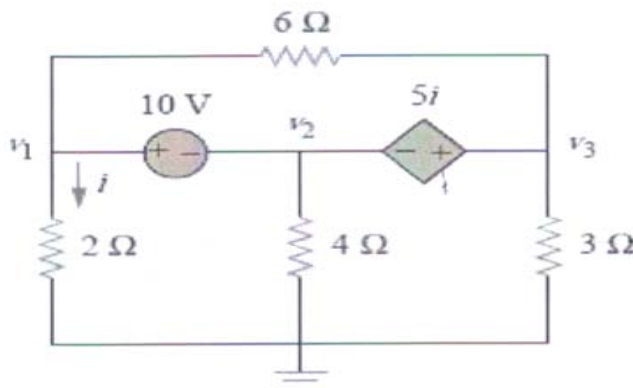- 7 Find V_1 , V_2 , V_3 using nodal analysis for the circuit shown in figure below.




UNIT - IV

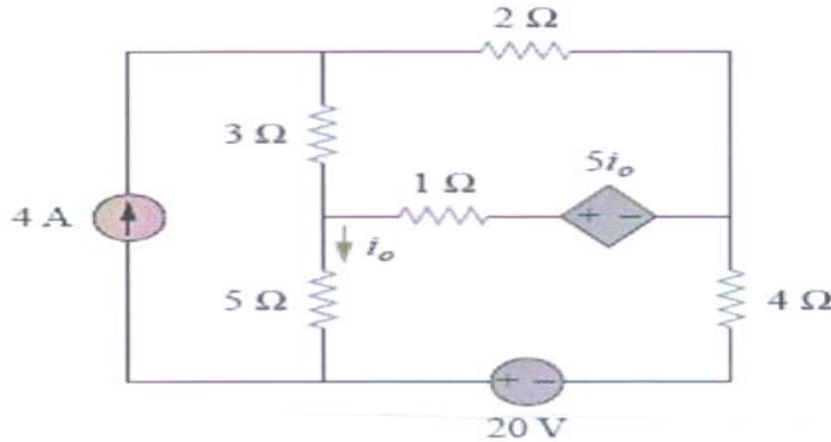- 8 Find I_0 for the circuit shown in figure below, using Superposition theorem.




OR

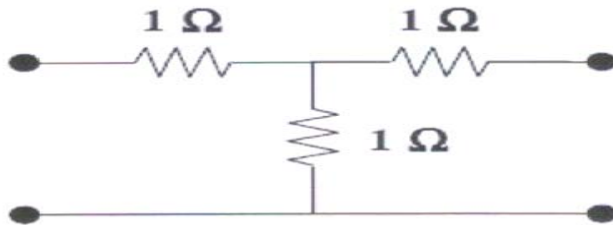- 9 Determine z-parameters for the circuit shown in figure below.



UNIT - V

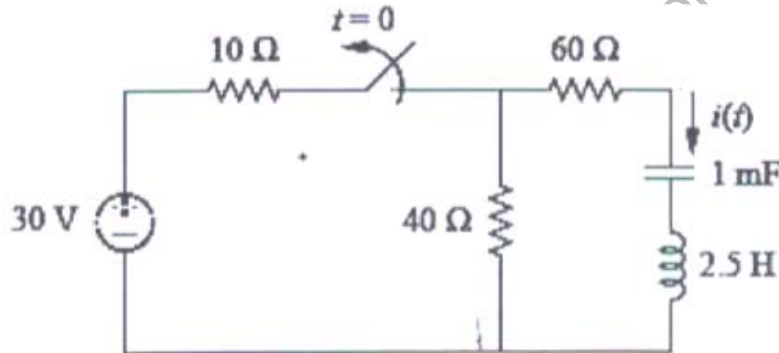- 10 Find $i(t)$ for $t > 0$ for the circuit shown in figure below.



OR

- 11 Determine the Fourier transform for the following functions:
(a) Gate function $u(t) - u(t - 1)$.
(b) $f(t) = te^{-2t}u(t)$.
