

Code: 13A04101

R13

B.Tech I Year (R13) Supplementary Examinations June 2017

NETWORK ANALYSIS

(Common to ECE & EIE)

Time: 3 hours

Max. Marks: 70

PART – A

(Compulsory Question)


- 1 Answer the following: (10 X 02 = 20 Marks)
- State superposition theorem.
 - Define cutset of a graph.
 - Define natural response of a network.
 - What is power factor?
 - What is the condition for resonance of an RLC series circuit?
 - Define coupling coefficient.
 - What are state variables?
 - What is the condition on transmission parameters for a reciprocal network?
 - What is a m-derived filter?
 - Define propagation constant.

PART – B

(Answer all five units, 5 X 10 = 50 Marks)


UNIT - I

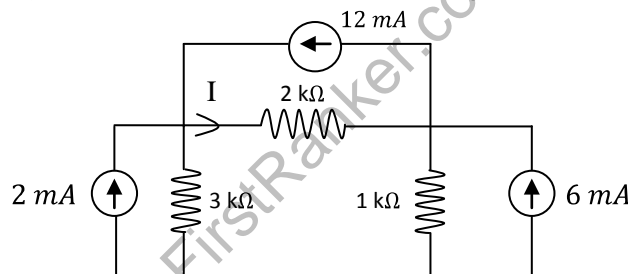- 2 By using nodal analysis find the current I in the following circuit.



OR

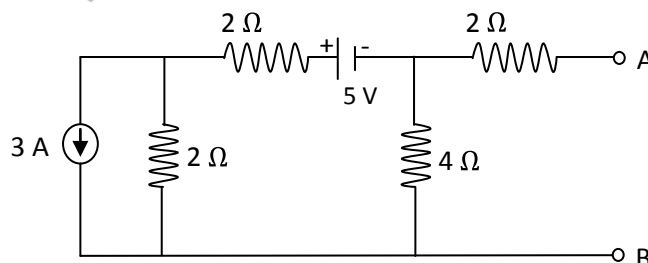- 3 Obtain Thevenin's equivalent for the circuit shown in figure below.



UNIT - II

- 4 Derive the source free response of RL circuit.
- OR**
- 5 The impedance of a circuit is $Z = (6 + j8)\Omega$ and the applied voltage is $V = 50\angle 45^\circ$ volts. Determine average & apparent powers & p.f.

Contd. in page 2

Code: 13A04101


R13

UNIT - III

- 6 Prove that for an RLC series circuit the resonant frequency is geometric mean of upper and lower half power frequencies.


OR

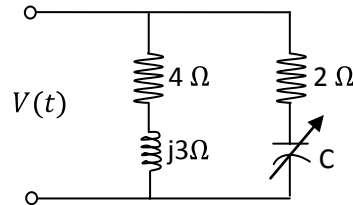- 7 Determine the value of C for which the circuit is resonant when $\omega = 2000$ rad/sec.




UNIT - IV

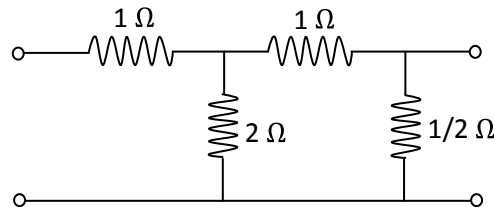- 8 Find the Y-parameters for the network shown in figure below.



OR

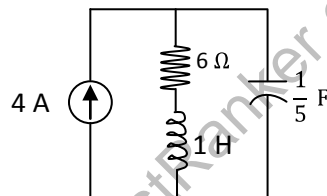- 9 Find the state variable equation for the circuit shown in figure below.



UNIT - V

- 10 Discuss the properties of symmetrical network.

OR

- 11 Design a m-derived low pass filter having cut-off frequency of 1 kHz, design impedance of 400Ω and the resonant frequency of 1100 Hz.
