

Code: 9A12301

B.Tech II Year I Semester (R09) Supplementary Examinations June 2017

DIGITAL LOGIC DESIGN & COMPUTER ORGANIZATION

(Common to CSS & IT)

Time: 3 hours

Max. Marks: 70

Answer any FIVE questions
All questions carry equal marks

- 1 (a) What is an error detection code? Write about error detection codes by giving examples.
(b) Convert the following numbers to decimal.
(1001001.011)₂, (12121)₃, (1032.2)₄, (4310)₅, (0.342)₆, (50)₇, (8.3)₉, (198)₁₂
- 2 (a) Design a 4-bit ring counter using D-Flip-flops and draw the circuit diagram and timing diagrams.
(b) Design a D-type positive edge triggered flip flop. Also show the operation of the sequential circuit when CP = 1.
- 3 What is an universal shift register? What are its capabilities? Design a 4-bit universal shift-register that has all the capabilities.
- 4 (a) Indicate the computational details of multiplying two 4-bit numbers 1011 and 0101 using Booth's algorithm. Verify the result obtained.
(b) Give the basic features of the IEEE floating point number standard.
- 5 (a) With the help of diagram, explain about interrupt cycle execution.
(b) Explain about IA-32 architecture supported addressing modes with examples.
- 6 (a) Explain how a word can be fetched from the memory using timing signals.
(b) Explain the implementation of one-bit register with a neat diagram.
- 7 (a) Discuss the Internal structure of 64 X 1 DRAM with help of a sketch.
(b) Explain the Timing diagram of the READ and WRITE cycle of Dynamic RAM.
- 8 (a) Explain hardware controlled data transfer with the help of a block diagram.
(b) Discuss the limitations of programmed I/O and interrupt driven I/O. Explain hardware controlled data transfer.
