

Code: 9A14301



B.Tech II Year I Semester (R09) Supplementary Examinations June 2017 ELECTRICAL ENGINEERING

(Mechatronics)

Time: 3 hours

Max. Marks: 70

Answer any FIVE questions All questions carry equal marks

5 can y

- 1 (a) State and explain Ohm's law.
 - (b) By taking any one example, state and explain Kirchoff's laws.
- 2 (a) Explain in detail the types of elements.
 - (b) Using superposition theorem, determine the current through 12 Ω resistor (all resistances are in Ω) as shown in figure below:



- 3 (a) Show that the power dissipated by a pure capacitor excited by a sinusoidal voltage source is zero.
 - (b) A series circuit consisting of a 10 Ω resistor, a 100 µF capacitance and a 10 mH inductance is driven by a 50 Hz AC voltage source of maximum value 100 V. Calculate the equivalent impedance, current in the circuit, the power factor and power dissipated in the circuit.
- 4 (a) Explain the constructional details of transformer.
 - (b) A single phase transformer working at unity power factor has an efficiency of 90% at both one half loads and at the full load of 500 W. Determine the efficiency at 75% of full load.
- 5 (a) Derive the e.m.f equation of DC generator.
 - (b) The armature of a 2-pole, 220 V Lap wound generator has 400 conductors and runs at 300 rpm. Calculate the useful flux/pole, if the number of turns in each field coil is 1200.
- 6 (a) Explain the losses that occur in a DC machine.
 - (b) A 4-pole, shunt motor has 472 wave connected armature conductors. The flux per pole for a field current of 2 A is 36 mWb and for 4 A is 42 mWb. The field resistance is 125 ohm. Calculate the no-load speed of the motor with a terminal voltage of 500 V.
- 7 (a) Explain the principle of operation of 3-phase induction motor.
 - (b) A 6 pole, 3-φ induction motor runs at 1140 rpm on full load when supplied from a 60 Hz supply. Determine the synchronous speed and slip at full load.
- 8 (a) Explain the essential features of measuring instruments.
 - (b) Explain the principle and operation of moving iron meters with neat diagram.
