

B.Tech II Year I Semester (R13) Supplementary Examinations June 2017

ELECTRICAL CIRCUITS

(Electrical and Electronics Engineering)


Time: 3 hours

Max. Marks: 70

PART – A
(Compulsory Question)

1 Answer the following: (10 X 02 = 20 Marks)

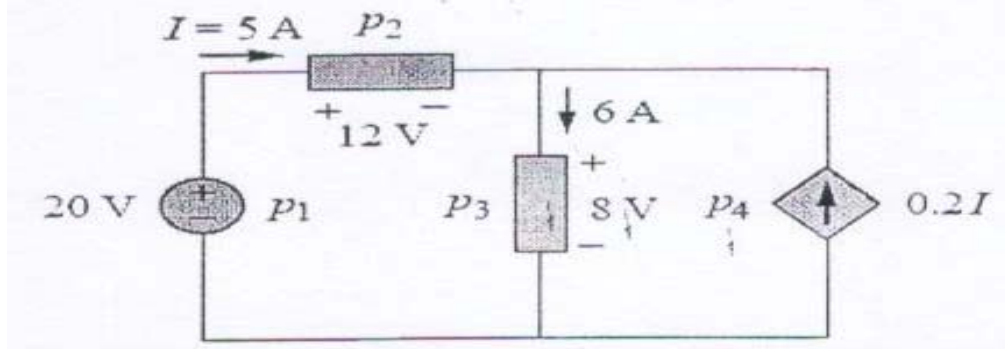(a) Calculate the power supplied and absorbed by the each element shown in below figure.




- (b) Derive the expression for the total inductance in series aiding connection.
- (c) Calculate the phase angle between $V_1 = -10 \cos(\omega t + 50^\circ)$ and $V_2 = 12 \sin(\omega t - 100)$. State which sinusoid is leading.
- (d) Define balanced voltage, phase sequence & balanced load.
- (e) Derive the expression for bandwidth and Q-factor for a series resonant circuit.
- (f) Define duality and briefly explain about the dual networks.
- (g) State reciprocity and compensation theorems.
- (h) What is a two port network? Explain the significance of two port network.
- (i) Find the Laplace transforms for: (i) The ramp function. (ii) $e^{at} u(t)$.
- (j) What is half-wave symmetry? Explain.

PART – B
(Answer all five units, 5 X 10 = 50 Marks)


UNIT – I

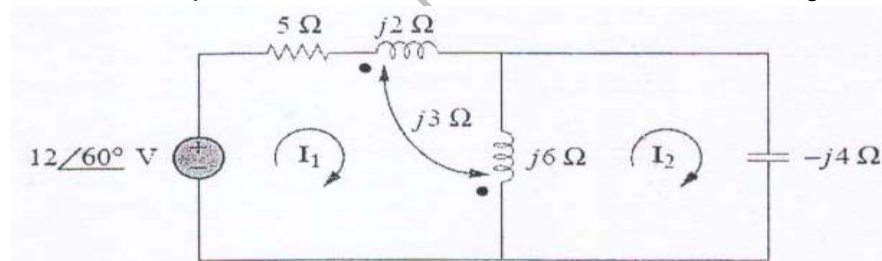2 Determine the phasor currents I_1 and I_2 for the circuit shown in figure below.



OR

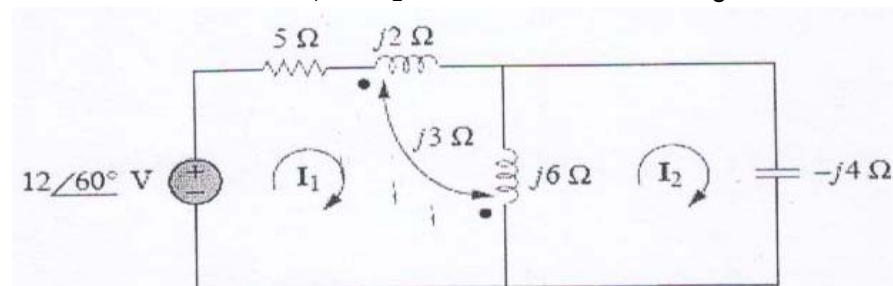
3 Determine the currents I_1 and I_2 for the circuit shown in figure below.



Contd. in page 2

UNIT – II

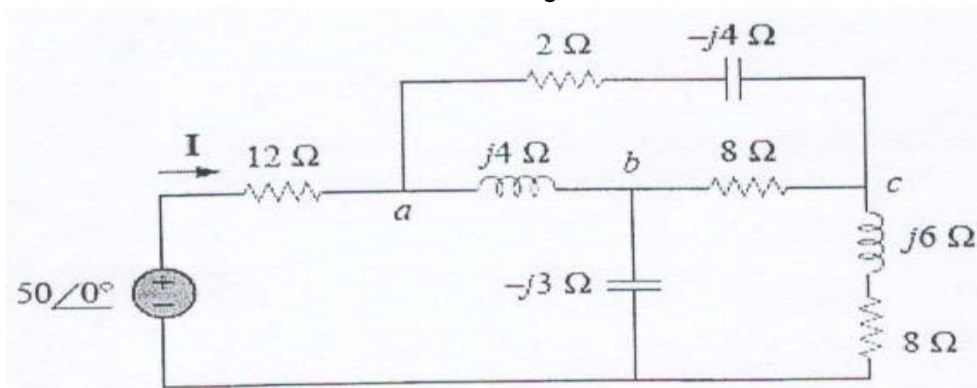- 4 Determine current I in the circuit shown in figure below.




OR

- 5 A Y-connected balanced 3-phase generator with an impedance of $0.4 + j0.3\Omega$ per phase is connected to a Y-connected balanced load with an impedance of $24 + j19\Omega$ per phase. The line joining the generator and the load has an impedance of $0.6 + j0.7\Omega$ per phase. Assuming a positive sequence for the source voltages and that $V_{an} = 120 \angle 30^\circ$. Find: (i) Line voltages. (ii) Line currents.


UNIT – III

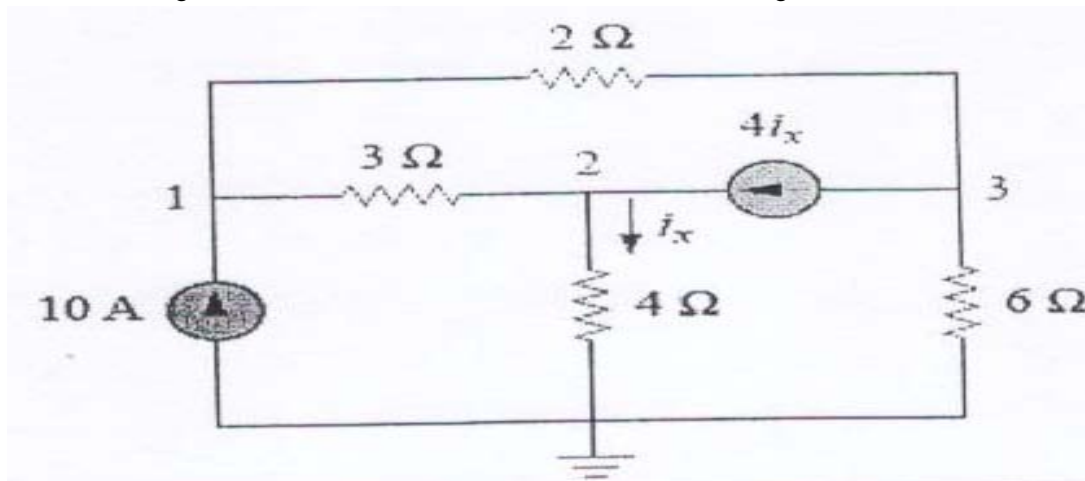- 6 Find the voltages at the three non reference nodes shown in figure below with the nodal analysis.



OR

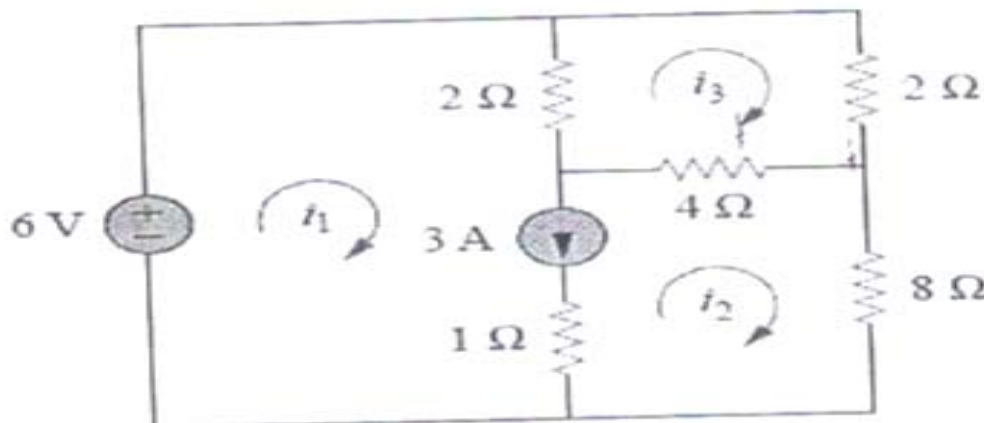
- 7 Using Mesh analysis determine i_1 , i_2 , i_3 for the circuit shown in figure below.



Contd. in page 3


UNIT – IV

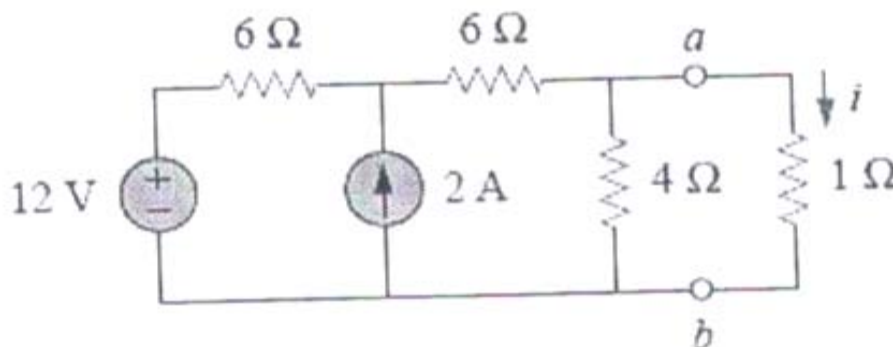- 8 Using Thevenin's circuit find I for the circuit shown in figure below.




OR

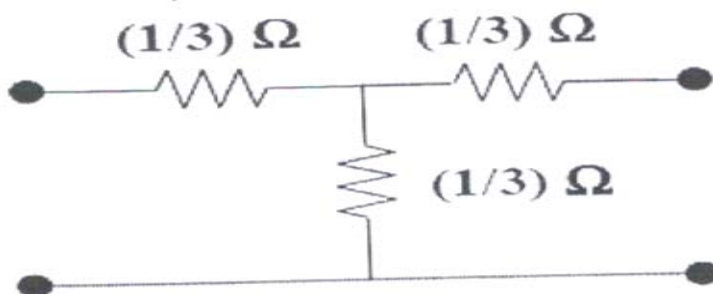- 9 Determine Y-parameters for the network shown in figure below.



UNIT – V

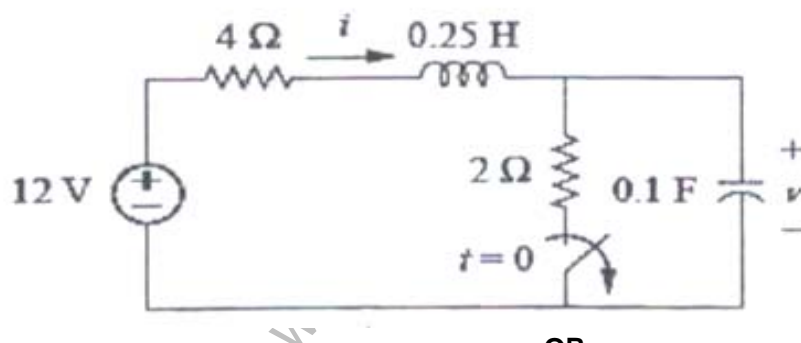- 10 The switch has been closed for a long time. It is open at $t = 0$ as shown in figure given below. Find: (i) $i(0+)$, $v(0+)$. (ii) $di(0+)/dt$, $dv(0+)/dt$. (iii) $i(\infty)$, $v(\infty)$.



OR

- 11 Calculate the Fourier transform of the signal shown in figure below.

