

B.Tech II Year I Semester (R15) Supplementary Examinations June 2017

ELECTRICAL CIRCUITS – II

(Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 70


PART – A
(Compulsory Question)

- 1 Answer the following: (10 X 02 = 20 Marks)
- The current in the inductor is given by $i(t) = \frac{1}{L} \int_0^t v(t) dt + i(0^+)$. Write equivalent domain expression.
 - Draw the time response of the current in a series RC circuit.
 - Draw phasor diagram of currents in 3-phase delta connected system.
 - What are the advantages of 3-phase system over other systems?
 - Write the properties of Fourier transform.
 - Write the exponential form of Fourier series.
 - Write the properties of incidence matrix.
 - What is duality in electrical engineering?
 - What are the properties of filters?
 - How the basic elements are presented in simulation environment.

PART – B
(Answer all five units, 5 X 10 = 50 Marks)

UNIT – I

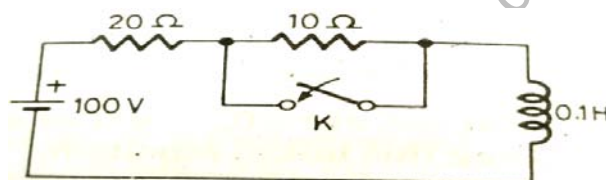- 2 (a) Derive an expression for transient response in RC series circuit with DC excitation.
(b) A DC voltage of 100 V is applied to the circuit shown in figure below and the switch K is open. The switch K is closed at $t = 0$. Find the complete expression for the current.



OR

- 3 (a) Write equation for voltage in a RLC series circuit.
(b) The winding of an electromagnet has an inductance of 3H and a resistance of 15 Ohms. When it is connected to a 120 V d.c. supply, calculate: (i) The steady state value of current flowing in the winding. (ii) The time constant of the circuit. (iii) The value of the induced e.m.f. after 0.1s.

UNIT – II

- 4 A Delta connected load has a parallel combination of resistance 5 ohms and capacitive reactance of $-j5$ ohms in each phase. If the balanced 3-phase 400 V supply is applied between lines, find the phase currents and line currents and draw the phasor diagram.


OR

- 5 Three impedances Z_A , Z_B and Z_C are connected in star across a 100 V, 50 Hz balanced 3-phase supply. Assuming $Z_A = 50 \angle 0^\circ \Omega$, $Z_B = j10 \Omega$, $Z_C = -j10 \Omega$, find the drop across each impedance and the potential of the neutral.

Contd. in page 2


UNIT - III

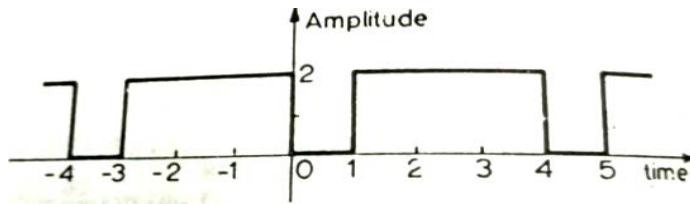- 6 Obtain the Fourier Series for the waveform shown in figure below.




OR

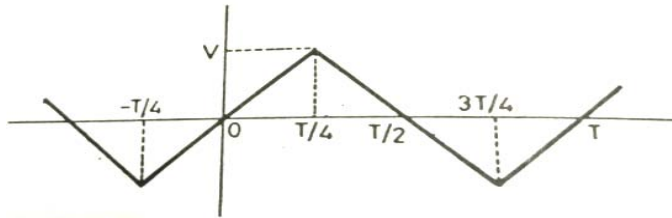- 7 Obtain the Fourier Series for the waveform shown in figure below.




UNIT - IV

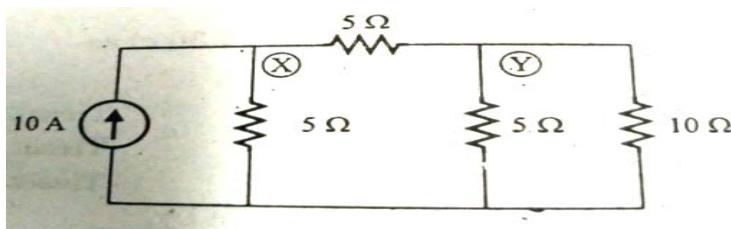- 8 Write cutest matrix, obtain the equilibrium equations using nodal equations for the network shown in figure below. Also find the Node voltages at X and Y using network topology.



OR

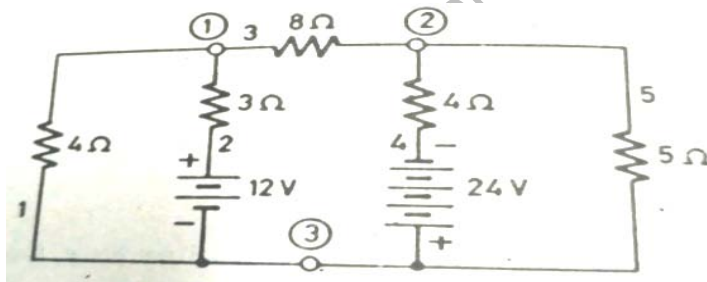- 9 For the network shown in figure below, write tie set matrix, write equilibrium equations and obtain the loop currents using network topology.



UNIT - V

- 10 Design a constant K-low pass filter having cut-off frequency 2.5 kHz and design resistance $R_0 = 700 \Omega$. Also find the frequency at which this filter produces attenuation of 19.1dB. Find its characteristic impedances and phase constant at pass band and stop or attenuation band.

OR

- 11 Solve the circuit using PSpice program.

