

B.Tech II Year I Semester (R15) Supplementary Examinations June 2017

ELECTRONIC DEVICES AND CIRCUITS

(Common to EEE, ECE and EIE)

Time: 3 hours

Max. Marks: 70

PART – A
(Compulsory Question)

- 1 Answer the following: (10 X 02 = 20 Marks)
- Differentiate drift and diffusion currents?
 - What is the operating principle of LED? Which colour of light is emitted by GaAs, Gp, GaAsp?
 - Discuss briefly about different filters.
 - Explain diode rectifier for power supply.
 - Explain the transistor operation with the help of four regions.
 - Write the differences between JFET & BJT.
 - What is the basic difference between bias compensation and stabilization?
 - If a transistor has α of 0.97, find the value of β . If $\beta = 200$, find the value of α .
 - Why we use h-parameters to describe a transistor?
 - Explain base width modulation of a transistor.

PART – B
(Answer all five units, 5 X 10 = 50 Marks)

UNIT – I

- 2 (a) Give diode current equation. Mention any two applications of a diode.
(b) Explain the operation of LCD. Mention its applications.

OR

- 3 (a) Discuss about V-I characteristics of tunnel diode with help of Fermi level diagram.
(b) Discuss diode capacitances with the help of equations.

UNIT – II

- 4 (a) A $50\ \Omega$ load resistance is connected across a half wave rectifier. The input supply voltage is 230 V (rms) at 50 Hz. Determine the DC output (average) voltage, peak-to-peak ripple in the output voltage (V_{p-p}), and output ripple frequency (f_r).
(b) Explain full wave rectifier with capacitor filter and derive expression for capacitor.

OR

- 5 (a) In the full-wave rectifier circuit, the transformer has a turns ratio of 1:2. The transformer primary winding is connected across an AC source of 230 V (rms), 50 Hz. The load resistor is ~~50~~ $50\ \Omega$. For this circuit, determine the DC output voltage, peak-to-peak ripple in the output voltage, and output ripple frequency.
(b) Explain the working principle of Bridge rectifier with derivations. Differentiate with Full Wave Rectifier.

UNIT – III

- 6 (a) Explain in detail about the Ebers Moll model. Describe base spread resistance.
(b) Explain the operation of JFET. Write some applications for JFET.

OR

- 7 (a) Explain the operation of BJT. Give the relationship between α , β and γ of a transistor.
(b) Compare MOSFET with JFET.

Contd. in page 2

UNIT – IV

- 8 (a) What is DC load line and AC load line? Explain the criteria for fixing operating point.
(b) Discuss about self bias circuit and derive expression for stability factor.

OR

- 9 (a) Discuss about collector to base bias circuit and derive expression for stability factor.
(b) Briefly explain about FET biasing.

UNIT – V

- 10 (a) Describe the determination of h-parameters of a transistor.
(b) Draw the basic CE amplifier circuit and its equivalent h-parameter model. Derive an expression for its R_i and R_o .

OR

- 11 (a) Draw the CS amplifier with self-bias and bypass resistor R_s . Derive the expressions for R_i , A_v , R_o , using its equivalent circuit.
(b) Explain about relation between h-parameters of CE, CB, CC configurations.

www.FirstRanker.com