

Code: 9A02401

B.Tech II Year II Semester (R09) Supplementary Examinations May/June 2017

**PRINCIPLES OF ELECTRICAL ENGINEERING**

(Common to EIE, E.Con.E, ECE &amp; ECC)


Time: 3 hours

Max. Marks: 70

Answer any FIVE questions  
All questions carry equal marks

\*\*\*\*\*

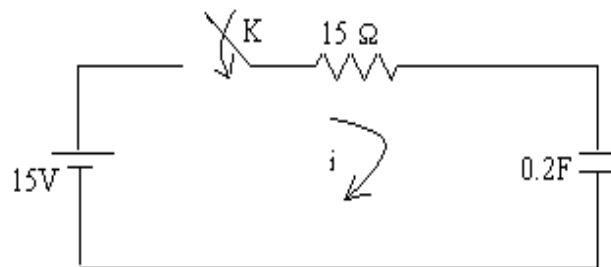- 1 A series RC circuit consists of  $R = 15 \Omega$  and  $C = 0.2 \text{ F}$  as shown in fig below. A constant voltage of  $15 \text{ V}$  is applied at  $t = 0$ . Obtain the current equation. Derive the equation for current and determine the voltage across the resistor and the voltage across the capacitor.



- 2 (a) Define and obtain Open circuit impedance parameters by taking any one example.  
(b) A two port network has the following parameters:  $Z_{11} = 20 \Omega$ ,  $Z_{12} = 5 \Omega$ ,  $Z_{21} = 20 \Omega$  and  $Z_{22} = 15 \Omega$ . Calculate short circuit parameters.
- 3 (a) Write short notes on Band-stop filters.  
(b) Design a prototype band stop filter section having cut-off frequencies of  $2000 \text{ Hz}$  &  $5000 \text{ Hz}$  and design resistance of  $600 \Omega$ .
- 4 What is an attenuator? What are the types of attenuators? Explain any two types of attenuators by deriving necessary equations.
- 5 A long-shunt compound generator supplies a load at  $200 \text{ V}$  through a pair of feeders of total resistance  $0.04 \text{ ohm}$ . The load consists of four motors, each taking  $50 \text{ A}$  and a lighting load of  $100$  bulbs each of  $50 \text{ W}$ . The armature resistance is  $0.03 \text{ ohm}$ , series field resistance  $0.04 \text{ ohm}$  and shunt field resistance  $40 \text{ ohm}$ .  
Find: (i) Load current.  
(ii) Terminal voltage.  
(iii) emf generated.
- 6 A  $200 \text{ V}$  dc shunt motor develops an output of  $16.9 \text{ kW}$  when taking an input of  $20.2 \text{ kW}$ . The field winding resistance is  $50 \text{ ohm}$  and armature resistance is  $0.06 \text{ ohm}$ . Calculate the efficiency and power input when the output is  $7.35 \text{ kW}$ .
- 7 Explain the constructional details of a single phase transformer.
- 8 (a) Explain the principle of operation of Shaded pole motor.  
(b) Explain the characteristics of Synchronos.

\*\*\*\*\*