

Code: 9A02405

B.Tech II Year II Semester (R09) Supplementary Examinations May/June 2017

ANALOG ELECTRONIC CIRCUITS


(Electrical & Electronics Engineering)

Time: 3 hours

Max. Marks: 70

Answer any FIVE questions
All questions carry equal marks

- 1 Derive all components in the Hybrid- π model in terms of h-parameters in CE configuration.
- 2 (a) What is diffusion capacitance of a transistor and derive its equation.
(b) In a given germanium PNP transistor, base width is 10^{-4} cm. At room temperature and for a dc emitter current of 2mA, find emitter diffusion capacitance and gain-band width product.
- 3 (a) Classify the feedback amplifiers and draw block diagrams.
(b) The open loop gain of an amplifier is 50 and its output impedance is 40 k Ω . When a negative feedback is applied, the output impedance becomes 6.666 k Ω . Find the feedback factor.
- 4 Derive the frequency of oscillations of the circuit shown in figure.

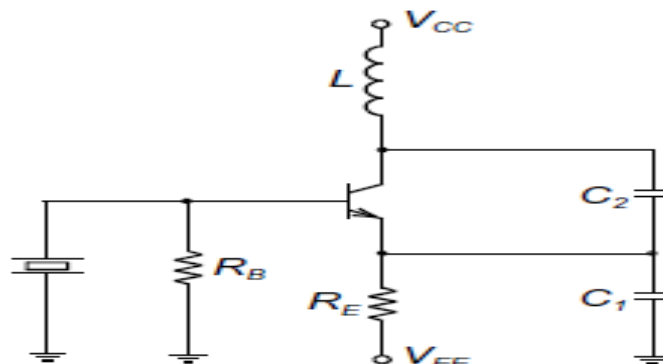

- 5 (a) Write short notes on requirement and types of heat sinks for power dissipation in large signal amplifiers.
(b) With the help of a neat circuit diagram, explain the operation of a complementary symmetry configured class-B power amplifier.
(c) Compare and contrast push-pull and complementary-symmetry configurations for class-B power amplifiers.
- 6 (a) What is synchronized clamping? Explain.
(b) Design a diode clamper circuit to clamp the positive peaks of the input signal at zero level. The frequency of the input signal is 500 Hz.
- 7 (a) Explain the reverse recovers of a semiconductor diode. How does the recovery time place a limitation on the diode speed?
(b) Write about diode switching times.
- 8 Calculate the stable state currents and voltages for the self biased bistable multivibrator which uses n-p-n silicon transistors. The various parameters for the circuit are: $V_{CC} = 12$ V, $R_1 = 30$ k Ω , $R_c = 4$ k Ω , $R_2 = 10$ k Ω and $R_E = 500$ Ω .
