

Code: 9A02406

B.Tech II Year II Semester (R09) Supplementary Examinations May/June 2017

NETWORK THEORY


(Electrical & Electronics Engineering)

Time: 3 hours


Max. Marks: 70

Answer any FIVE questions
All questions carry equal marks


- 1 (a) Explain the single watt meter method measurement of power with a neat diagram.
(b) Three coils each having a resistance of 20Ω and an inductive reactance of 15Ω are connected in star and fed by a 3-phase, 400 V, 50 Hz system. Find (i) Line current. (ii) Power. (iii) Power factor.
- 2 The power flowing in 3- Φ , 3 wire balanced load system is measured by the two-wattmeter method. The reading of wattmeter A is 4000 W and on wattmeter B is -1000 W. What is the power factor of the system and also derive the expression for power factor?
- 3 A series RL circuit with $R = 20 \Omega$ and $L = 10H$ has a constant voltage, $V = 50 V$ applied at $t = 0$ as shown in fig below. Derive the equation for current and determine the current i , the voltage across resistor and the voltage across inductor.

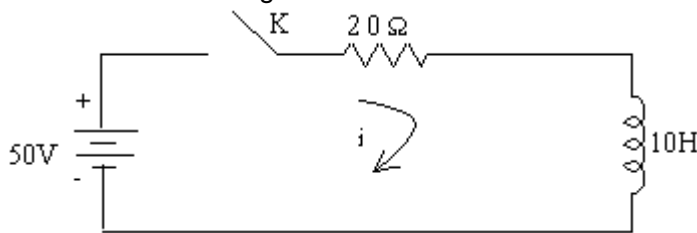

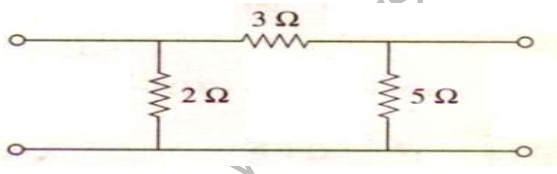- 4 A series R-C circuit has $R = 20 \Omega$ and $C = 100 \mu F$. A voltage $V = 200 \sin(314t)$ is applied at $t = 2.14$ m sec. Obtain an expression for ' i '. Also, find the value of current after time 1 m sec from the switching instant.
- 5 Find the z-parameters for the circuit shown below:



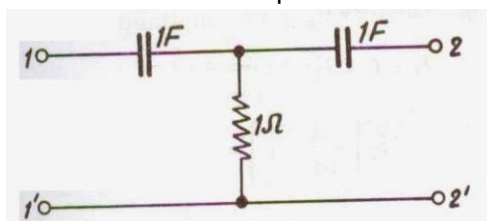- 6 Find the transmission parameters for the following network:



- 7 Derive the Fourier series of a half-wave rectified sine wave.
- 8 (a) Define inverse Fourier transform.
(b) Find the inverse Fourier transform of $y(w) = \pi\delta(w) + \frac{1}{jw} + \frac{2(1+jw)}{(1+jw)^2 + 16}$.