

B.Tech II Year II Semester (R13) Supplementary Examinations May/June 2017

ANALOG ELECTRONIC CIRCUITS

(Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 70

PART – A
(Compulsory Question)

- 1 Answer the following: (10 X 02 = 20 Marks)
- What are the coupling schemes used in multistage amplifiers?
 - Two identical amplifiers having 10dB gain each are cascaded. Calculate the output, if the input is 1mV(pp).
 - What are the advantages of negative feedback?
 - Define the feedback factor.
 - Define Barkhausen criterion.
 - What is piezoelectric effect?
 - What is crossover distortion?
 - What is the use of heat sink?
 - Mention few applications of astable multivibrator.
 - What are different types of clippers?

PART – B

(Answer all five units, 5 X 10 = 50 Marks)

UNIT – I

- 2
- Explain low frequency and high frequency response of RC coupled amplifier.
 - Calculate overall lower 3dB and upper 3dB frequency for a 3-stage amplifier having an individual lower cut off frequency of 40 Hz and upper frequency of 2 MHz.

OR

- 3
- When 2-stages of identical amplifiers are cascaded, obtain the expressions for overall voltage gain, current gain and power gain.
 - Explain the advantages of cascading of amplifier configurations.

UNIT – II

- 4
- List the general characteristics of negative feedback amplifier and derive the expression for gain with negative feedback.
 - The voltage gain of an amplifier without feedback is 60dB. It decreases to 40dB with feedback. Calculate the feedback factor.

OR

- 5 Draw the circuit diagram of voltage shunt feedback amplifier and derive the expressions for voltage gain and feedback factor.

UNIT – III

- 6 With simple diagrams, explain Wein bridge oscillator and derive its frequency of oscillation.

OR

- 7 Explain Hartley oscillator and derive the equation for oscillation.

UNIT – IV

- 8 Draw the circuit diagram of class B push pull amplifier and explain its operation. Derive an expression for its maximum conversion efficiency.

OR

- 9
- Explain the classification of power amplifiers.
 - Explain the operation of transformer coupled class A amplifier and show that it has a maximum efficiency of 50%.

UNIT – V

- 10
- What is meant by linear wave shaping? Give some examples of linear wave shaping circuits.
 - Draw a high pass RC circuit and explain its response to a step input.

OR

- 11 With neat circuit diagram and waveforms, explain the operation of a monostable multivibrator and derive the expression for the pulse width.