

B.Tech II Year II Semester (R15) Regular Examinations May/June 2017

**ANALOG ELECTRONIC CIRCUITS**

(Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 70

**PART – A**  
(Compulsory Question)

\*\*\*\*\*

- 1 Answer the following: (10 X 02 = 20 Marks)
- (a) What are the advantages and limitations of RC coupled amplifier?
  - (b) What is cascaded amplifier?
  - (c) List out the four basic feedback topologies.
  - (d) Compare the input and output resistance of voltage and current shunt feedback amplifier.
  - (e) State Barkhausen criterion for an oscillator.
  - (f) How frequency stability can be improved in the oscillators?
  - (g) Briefly explain the working principle of push pull amplifier.
  - (h) Define heat sink.
  - (i) How RC circuit be used as a differentiator?
  - (j) Why monostable multivibrator is also called as delay circuit?

**PART – B**  
(Answer all five units, 5 X 10 = 50 Marks)

**UNIT – I**

- 2 Analyze the RC coupled amplifier in Low range, Mid-range and High range frequencies.

**OR**

- 3 Explain the operation of single stage amplifier with circuit diagram and determine its gain bandwidth product.

**UNIT – II**

- 4 Discuss the effects of negative feedback on gain, band width and distortion.

**OR**

- 5 Analyze the circuit and determine the input and output resistance of voltage series feedback amplifier.

**UNIT – III**

- 6 Derive an expression for frequency of oscillation for Colpitts oscillator and explain the operation of the same.

**OR**

- 7 Explain the working principle and operation of Wein bridge oscillator with diagram.

**UNIT – IV**

- 8 Discuss about the operation of transformer coupled amplifier with diagram. Write down the advantages of the same.

**OR**

- 9 Explain the working principle and operation of transformer-less class B power amplifier with diagram.

**UNIT – V**

- 10 Derive and draw the response of low pass RC circuit to the following waveforms. (i) Step. (ii) Square.

**OR**

- 11 With neat circuit diagram, explain the triggering of astable multi vibrator and derive its time period.

\*\*\*\*\*