

Code: 9A02504

B.Tech III Year I Semester (R09) Supplementary Examinations June 2017

**POWER ELECTRONICS**

(Common to EEE &amp; E.Con.E)

Time: 3 hours

Max. Marks: 70

Answer any FIVE questions  
All questions carry equal marks

\*\*\*\*\*

- 1 (a) State and explain various turn on methods of SCR.  
(b) Explain in detail the dynamic characteristics of an SCR are assumed to be a straight line passing through origin with a gradient of  $3 \times 10^3$ . Calculate the required gate source resistance. Given that  $E_{gs} = 10 \text{ V}$  and allowable  $P_g = 0.012 \text{ ohm}$ .
- 2 (a) Explain in detail the Resonant-Pulse Commutation.  
(b) Explain in detail the constructional details of IGBT.
- 3 (a) Describe the operation of a single phase two pulse midpoint converter with relevant waveforms. Derive an expression for average output voltage.  
(b) A single phase half controlled bridge converter is supplied at 230 V, 50 Hz with source inductance of 2mH. Neglecting resistance voltage drop, when the converter is operating at a firing angle of 45deg, and the load current is constant at 10 A. Determine the load voltage.
- 4 A 1-phase full converter feeding RLE has the following data source voltage is 230 V, 50 Hz,  $R = 2.5 \Omega$ ,  $E = 100 \text{ V}$  and firing angle is 30deg. Assume the output current is continuous of constant value. Evaluate: (i) Average value of load voltage and load current. (ii) Input power factor.
- 5 (a) Distinguish between three pulse and six pulse converters.  
(b) Explain the operation of three phase mid-point converter with associate waveforms.
- 6 Explain briefly
  - (a) AC Voltage controller.
  - (b) Cycloconverter.
  - (c) Traic.
- 7 (a) Derive an expression for output power for type D chopper.  
(b) Explain in detail the principle operation of the four quadrant chopper.
- 8 Explain the operation of basic series inverter with neat diagram? Compute the O/P frequency of a series inverter with the following specifications  $L = 10\text{mH}$ ,  $R = 150 \Omega$ ,  $T_{\text{off}} = 0.2 \text{ ms}$ . Also find the attenuation factor (AF).

\*\*\*\*\*