

Code: 9A10504

B.Tech III Year I Semester (R09) Supplementary Examinations June 2017

LINEAR & DIGITAL IC APPLICATIONS

(Common to E.Con.E, EIE & ECC)

Time: 3 hours

Max. Marks: 70

Answer any FIVE questions
All questions carry equal marks

- 1 (a) Explain the dc and ac characteristics of an opamp.
(b) Define the terms CMRR, slew rate and PSRR for an opamp.
- 2 (a) Draw the circuit diagram of an instrumentation amplifier using opamp and explain its operation.
(b) Explain with diagram, the working of a V to I converter with grounded load.
- 3 (a) Draw the block diagram of a phase locked loop and explain the principle of operation and function of each block.
(b) Explain the application of a PLL for frequency multiplication.
- 4 (a) Summarize the characteristic features of CMOS logic family.
(b) Explain the CMOS steady state electrical behavior.
- 5 (a) Draw the working of a basic TTL logic circuit and explain its working.
(b) Explain the interfacing of CMOS and TTL logic circuits.
- 6 (a) Describe the various statements used in behavioral modeling of VHDL.
(b) Explain the use of tasks and functions of VHDL.
- 7 (a) Explain the design of a 8 bit unsigned adder in VHDL.
(b) Explain the design of m by n decoder with its implementation in VHDL.
- 8 Draw the state table, state diagram and logic circuit of a 1 digit decimal up counter and explain its implementation in VHDL.
