

B.Tech III Year I Semester (R13) Supplementary Examinations June 2017

LINEAR & DIGITAL IC APPLICATIONS
(Electronics and Instrumentation Engineering)

Time: 3 hours

Max. Marks: 70

PART – A
(Compulsory Question)

- 1 Answer the following: (10 X 02 = 20 Marks)
- Define CMRR.
 - What do you mean by input offset current and offset voltage?
 - What is the difference between inverting and non-inverting amplifier.
 - List the applications of PLL.
 - Define the term noise margin.
 - What is meant by comparator?
 - What are the data types available in VHDL?
 - Write syntax of entity block in VHDL.
 - Define encoder and decoder.
 - Differentiate between latch and flip-flop.

PART – B
(Answer all five units, 5 X 10 = 50 Marks)

UNIT – I

- Explain the pole-zero compensation technique.
 - Explain about 741 Op-amp features.
- OR**

 - Explain the working of instrumentation amplifier.
 - Draw the equivalent circuit of the practical op-amp and explain the voltage transfer curve of the op-amp.

UNIT – II

- Explain how frequency multiplication is done using PLL.
 - Explain the working of voltage controlled oscillator.

OR

- With the help of neat internal functional diagram, explain the working of IC 555 as a Astable Multivibrator.

UNIT – III

- Explain sinking current and sourcing current of TTL output. Which of the parameters decide the fan-out and how?
 - Draw the resistive model of a CMOS inverter circuit and explain its behavior for LOW and HIGH outputs.

OR

- Explain TTL inverter operation with neat diagram and transfer characteristics.
 - Design a TTL two input NAND gate and explain the operation with the help of function table.

UNIT – IV

- Discuss the steps in VHDL design flow.
 - Explain the use of packages. Give the syntax and structure of a package in VHDL.

OR

- Write a behavioral style VHDL program for Barrel shifter.

UNIT – V

- Design Binary to Gray code converter and explain its procedure in detail.
 - Write about three state devices and Parity circuits.

OR

- Implement S-R flip flop using D-flip flop.
 - Write VHDL program for priority encoder.
