

B.Tech III Year II Semester (R09) Supplementary Examinations May/June 2017

POWER SYSTEM ANALYSIS
(Electrical & Electronics Engineering)

Time: 3 hours

Max. Marks: 70

Answer any FIVE questions
All questions carry equal marks

- 1 (a) What is a primitive network and represent its forms? Prove $Y_{Bus} = A^T[Y]A$ using singular transformation.
(b) Form the Y_{Bus} for the given network in table.

Element	R,p.u	X,p.u
1-2	0.05	0.15
1-3	0.10	0.30
2-3	0.15	0.45
2-4	0.1	0.30
3-4	0.05	0.15


- 2 (a) Explain the algorithm for the addition and removal of lines in power system.
(b) A two – Bus system has $Z_{Bus} = \begin{bmatrix} j0.11 & j0.045 \\ j0.045 & j0.13 \end{bmatrix}$ p.u if an impedance $Z_b = j0.06$ p.u. is connected between buses 1 and 2, what is the new Z_{Bus} .
3 Derive the basic equations for load flow studies and also write the assumptions and approximations to get the simple equations.
4 Consider the single line diagram of a power system shown in below. Take bus-1 as slack bus and the Y_{Bus} matrix is given below.

$$Y_{BUS} = \begin{bmatrix} 2 - j15 & -1 + j6 & -1.5 + j8 \\ -1 + j6 & 4 - j10 & -3 + j6 \\ -1.5 + j8 & -3 + j6 & 5 - j6 \end{bmatrix}$$

Scheduled generation and loads are as follows:


Bus no.	Generation		Load		Assumed bus voltages
	MW	MVAR	MW	MVAR	
1	0	0	0	0	1.04+j0.0
2	0	0	250	150	1.0+j0.0
3	100	70	50	20	1.0+j0.0

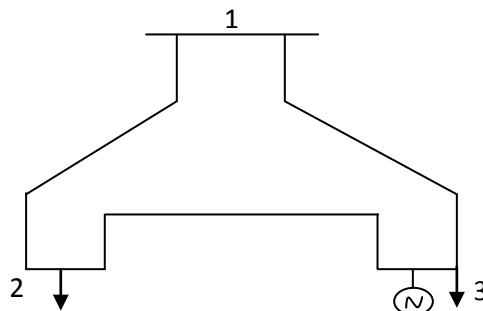Using Newton-Raphson method, obtain the bus voltages at the end of 1st iteration.




Contd. in page 2

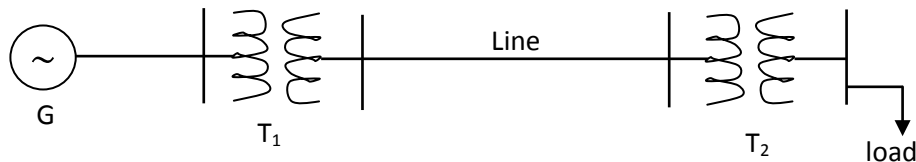- 5 Obtain pu impedance diagram of the power system of figure below. Choose base quantities as 15 MVA and 33 KV.
Generator: 30 MVA, 10.5 KV, $X'' = 1.6$ ohms.
Transformers T1 & T2: 15 MVA, 33/11 KV, $X = 15$ ohms referred to HV transmission line: 20 ohms/phase.
Load: 40 MW, 6.6 KV, 0.85 lagging p.f.



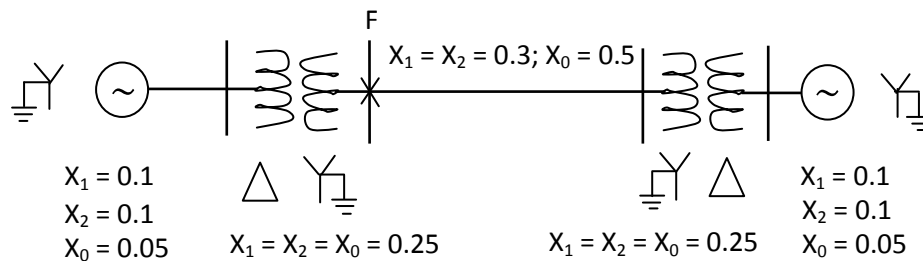- 6 For the system shown in figure below. A LLG fault occurs at point F. Find fault current.



- 7 A salient pole synchronous generator is connected to an infinite bus via a line. Derive an expression for electrical power output of the generator and draw $p - \delta$ curve.
- 8 Explain step-step method of solving the swing equation. Also write assumptions made.
